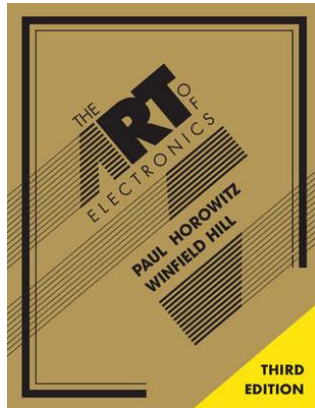


Analog electronics hands-on

- Analog – Digital?
- Recommended readings
 - for beginners
 - special topics
- How to proceed?
 - theory
 - modelling (simulations with LTspice IV)
 - experiments
- General topics
 - linear circuits – basic laws and tools
 - ideal operational amplifier
 - real operational amplifier - stability
 - basic circuits with operational amplifiers
 - comparators – discriminators
- Special topics for nuclear & high energy physicists
 - Pole/Zero correction and shaping amplifier
 - single channel analyzer
 - timing – leading edge, constant fraction discriminator

Recommended readings




The Art of Electronics

Paul Horowitz, Winfield Hill

<http://artofelectronics.net/>

Learning the Art of Electronics A Hands-On Lab Course

Thomas C. Hayes, Paul Horowitz

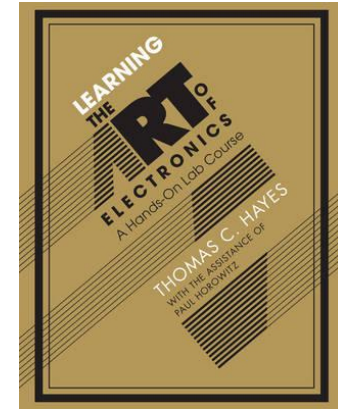


Halbleiter-Schaltungstechnik

Ulrich Tietze, Christoph Schenk,
Eberhard Gamm


<http://www.tietze-schenk.de/tsbuch.htm>

English version available:

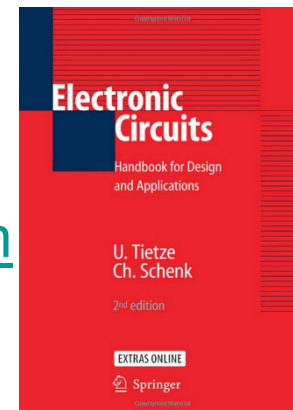Electronic Circuits: Handbook for Design and Application



Online available readings

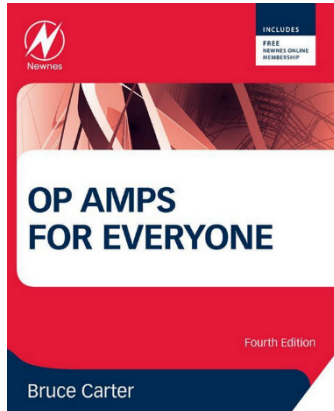



Op Amps for everyone (TI) – find it with google!

Handbook of Operational Amplifier Applications - Texas Instruments

www.ti.com/lit/an/sboa092a/sboa092a.pdf

Op Amp Applications Handbook (AD)

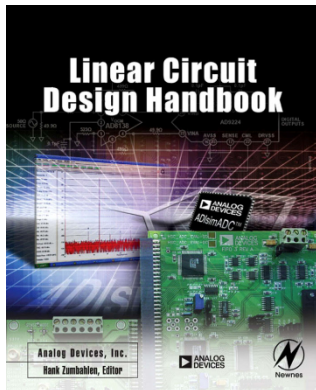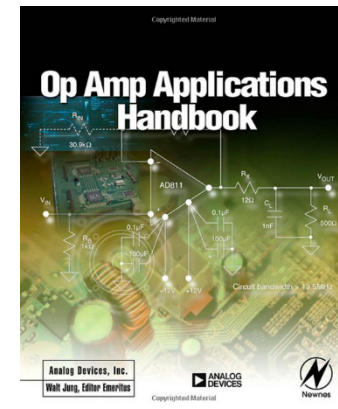
http://www.analog.com/library/analogDialogue/archives/39-05/op_amp_applications_handbook.html



Linear Circuit Design Handbook (AD)

http://www.analog.com/library/analogDialogue/archives/43-09/linear_circuit_design_handbook.html

Special topics


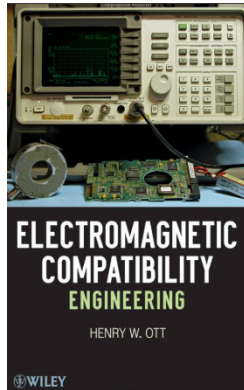


Electromagnetic Compatibility Engineering



Henry W. Ott

Everything about cabling, grounding, shielding, noise, PCB layout problems!

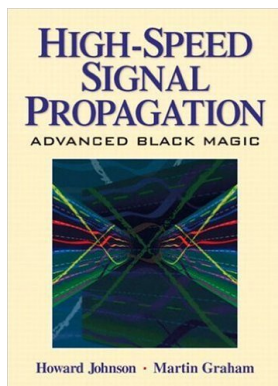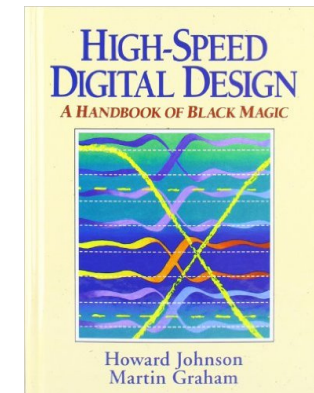High Speed Digital Design: A Handbook of Black Magic and High Speed Signal Propagation: Advanced Black Magic
by Howard Johnson, Martin Graham



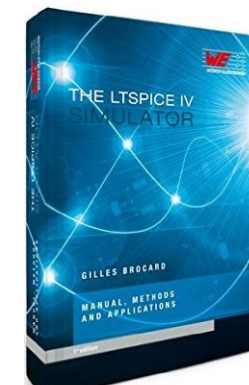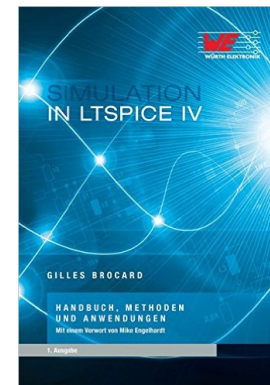**Simulation in LTspice IV
or
The LTspice IV Simulator**
by Gilles Brocard Würth



Lets start with some known laws from the physics

... and some useful techniques to analyse electric circuits


- Ohm's law
- Kirchhoff's laws
 - Algebraic sum of currents in and out of a node is 0
 - Algebraic sum of voltage drops in a closed loop is 0
- Mesh analysis
- **Only for linear circuits:**
 - **Norton and Thévenin theorems**
 - **Superposition**

Linear circuits


- Ideal and real voltage and current sources
 - Thévenin and Norton theorems
- Equivalent transformations
- Examples
- AC circuits
 - Low pass, high pass filter
- Impedance matching, termination (experimental)

Ideal and real sources, source transformations – Thévenin & Norton Theorems

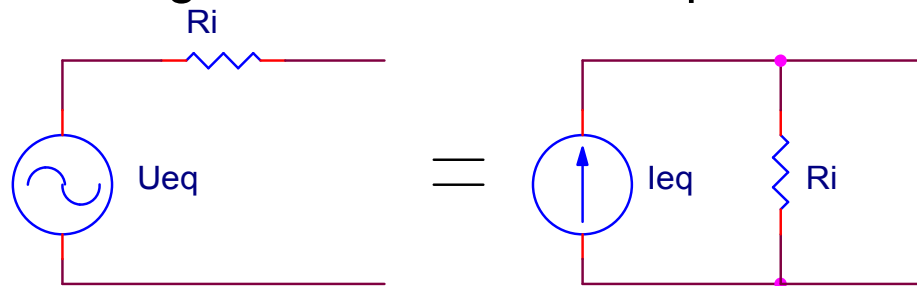- Ideal & real voltage/current sources, equivalence (Norton theorem)



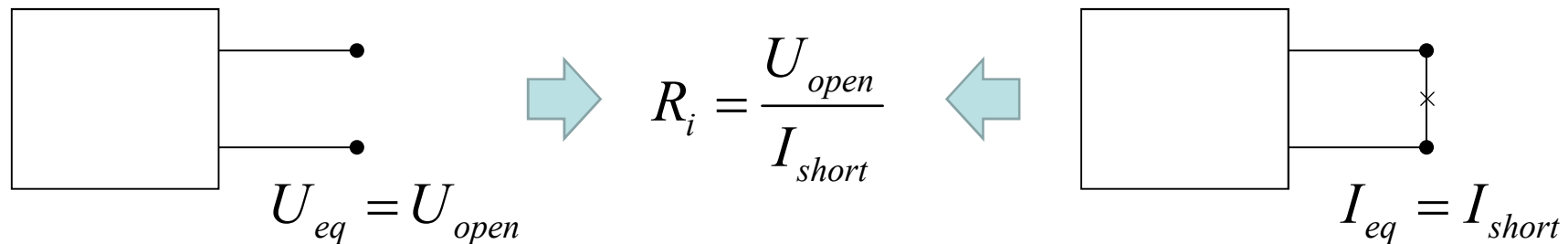
- Thévenin-Theorem for a two terminal part of a circuit



Not recommended as experimental method!!!

R_i can be found by removing all current sources and setting all voltage sources to 0, then it is the resistance seen at the two terminals.

Example: voltage divider

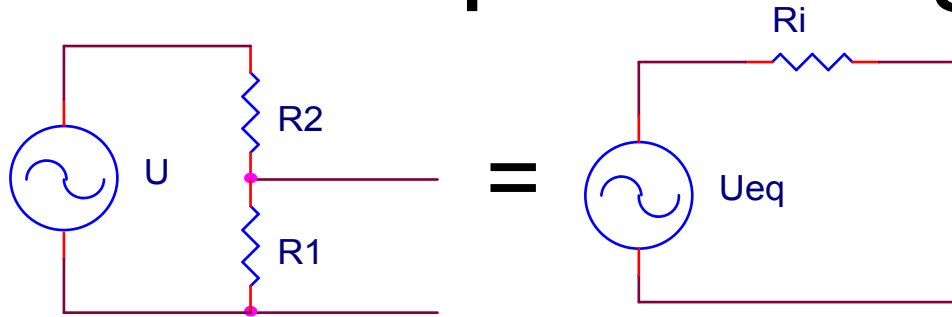

$$U_{eq} = U_{open} = U \frac{R_1}{R_1 + R_2}$$


$$I_{short} = \frac{U}{R_2}$$

$$R_i = \frac{U_{open}}{I_{short}} = \frac{U \cdot R_1}{\frac{U \cdot R_1}{R_1 + R_2}} = \frac{R_1 + R_2}{1} = R_1 + R_2$$

$$= \frac{R_1 \cdot R_2}{R_1 + R_2} = R_1 \parallel R_2$$

Alternative:

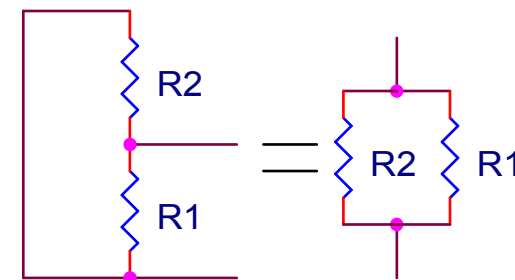- set $U=0$
- calculate the resistance seen from outside:



$$R_i = R_1 \parallel R_2$$

Example: loaded voltage divider

- May I load the voltage divider?



$$U_{eq} = U \frac{R_1}{R_1 + R_2}$$

$$I = \frac{U_{eq}}{R_L + R_i}$$

$$R_i = R_1 \parallel R_2$$

$$U_{RL} = U_{eq} - I \cdot R_i$$

Example

$$U = 10V, R_1 = 1k, R_2 = 9k$$

$$U_{eq} = 1V, R_i = 0.9k$$

$$R_L = 100k, I = 1V / 100.9k = 9.9\mu A$$


$$I_{R1,R2} = 1mA = 1000\mu A$$

$$rel.err \approx R_i / R_L$$

$$rel.err. \approx 0.9k / 100k \approx 1\%$$

Example: circuit transformations

- Which is the current through R?

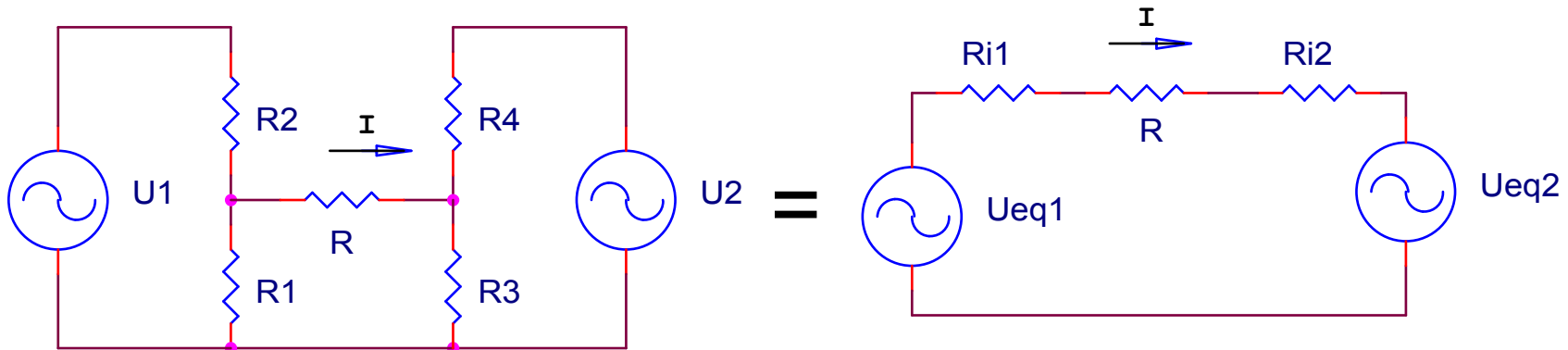

$$R_{i1} = R_1 \parallel R_2$$

$$R_{i2} = R_3 \parallel R_4$$


$$U_{eq1} = U_1 \frac{R_1}{R_1 + R_2}$$

$$U_{eq2} = U_2 \frac{R_3}{R_3 + R_4}$$


$$I = \frac{(U_{eq1} - U_{eq2})}{R_{i1} + R_{i2} + R}$$

Superposition principle

- What is the voltage in the middle?




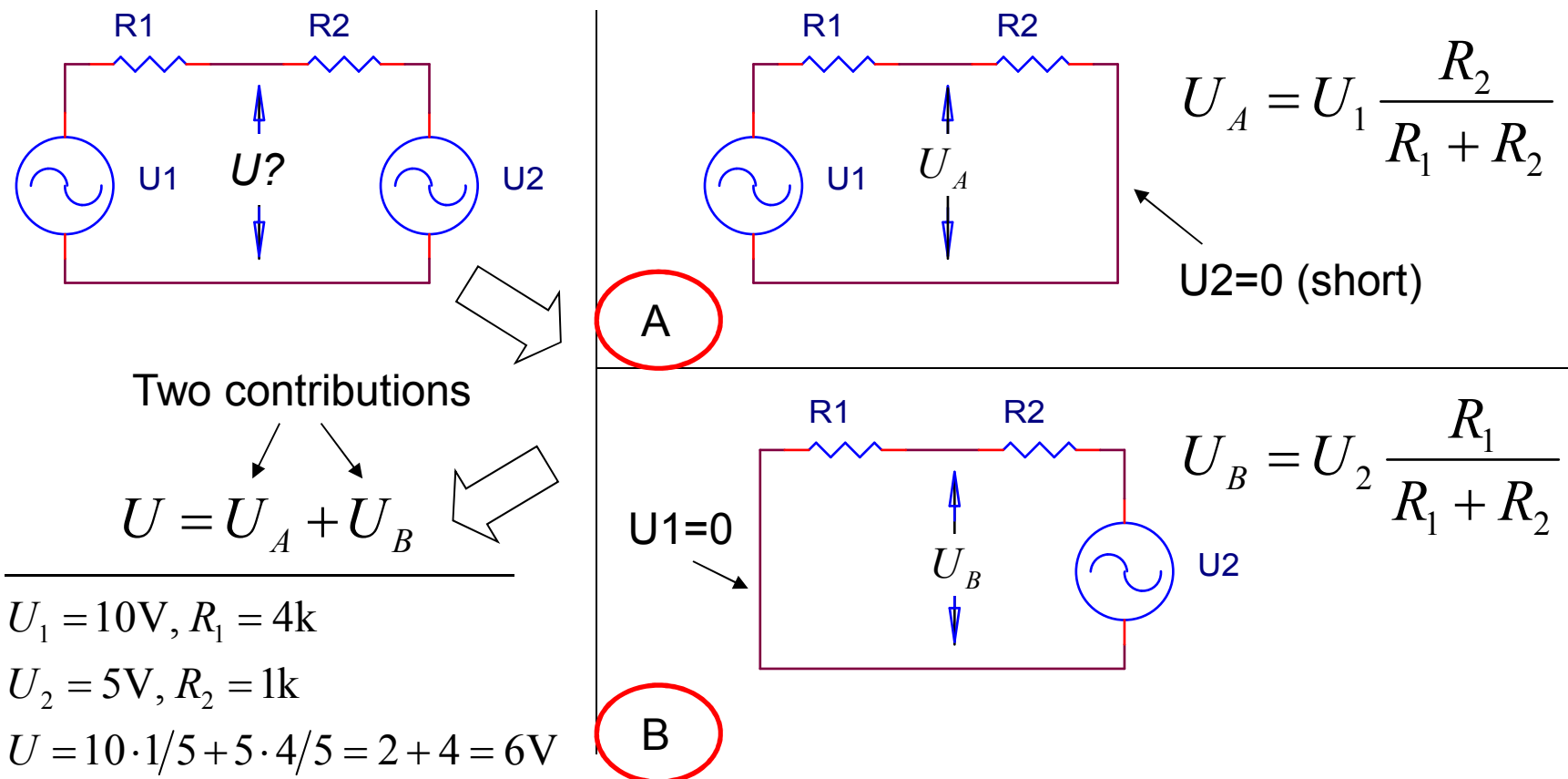


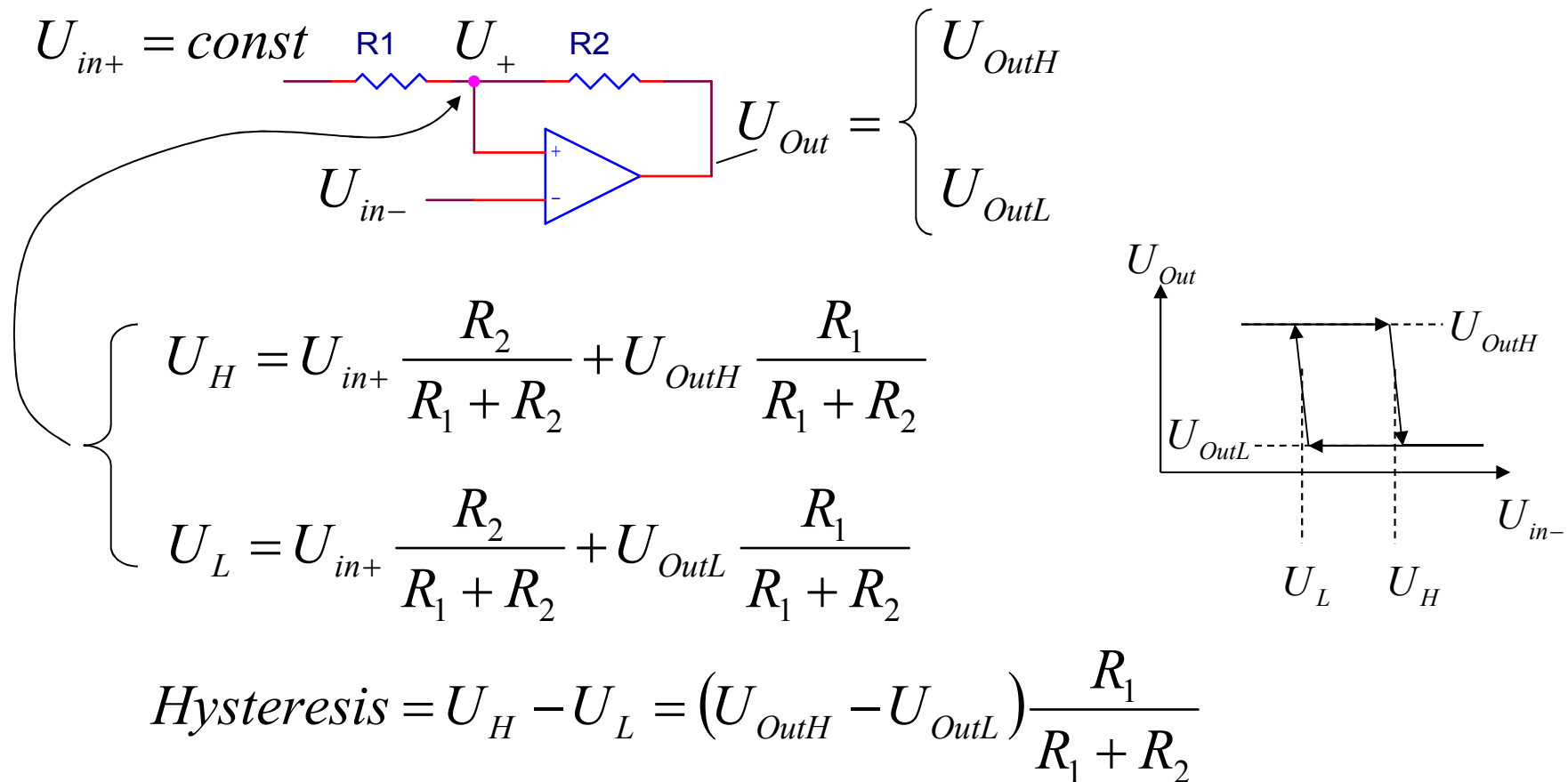Superposition principle example - Comparator with Hysteresis



Example $R_1 = 1\text{k}, R_2 = 50\text{k}, U_{out} = 0 \mid 5\text{V}, \text{Hyst.} = (1/51) \cdot 5\text{V} = 98\text{mV} \approx 100\text{mV}$


Example - R-2R Network

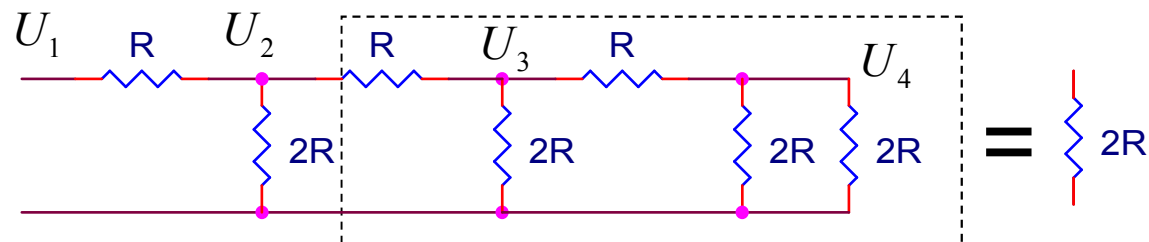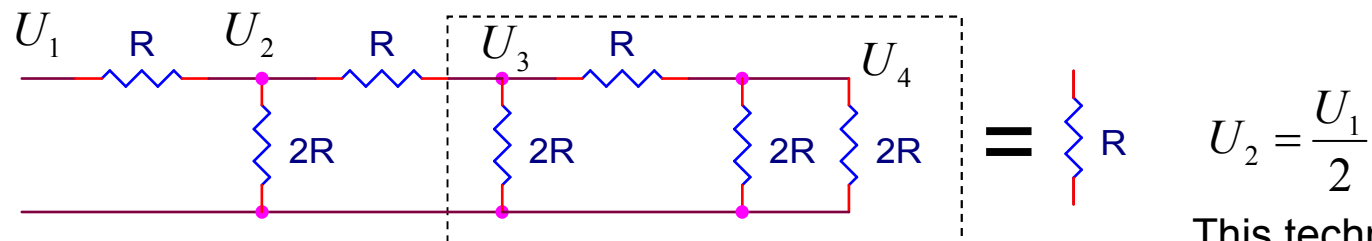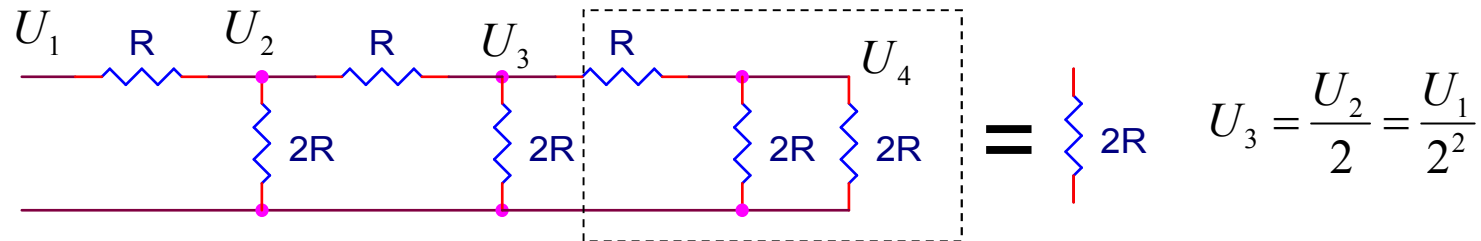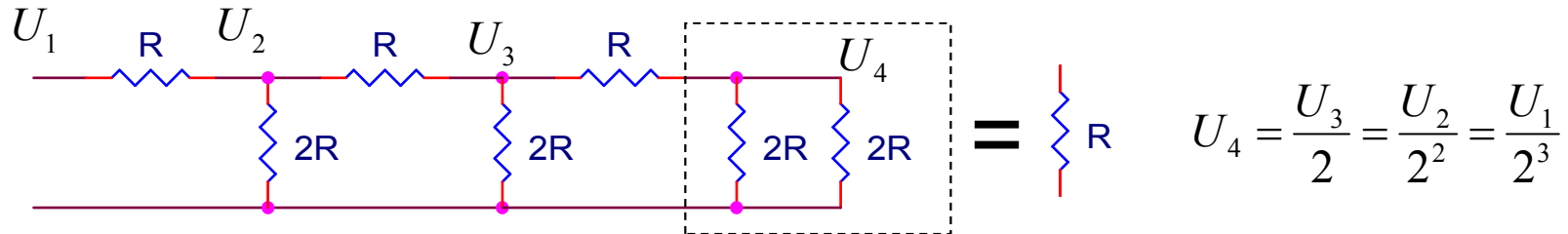

usw.

This technique is used in digital to analogue converter to divide the reference voltage using only two values of the resistors.

Example – T-attenuator

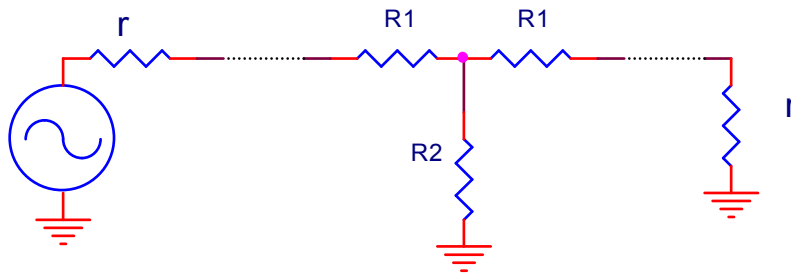

$$Z_{IN} = Z_{OUT} = (r + R_1) \parallel R_2 + R_1 = r$$

The attenuation only of the T-net is

$$\frac{R_2}{r + R_1 + R_2}$$

Note that the attenuation without the T-net is $\frac{1}{2}$, so the total attenuation with proper termination is

$$G = \frac{1}{2} \cdot \frac{R_2}{r + R_1 + R_2}$$

- The signal source has output impedance $r=50\Omega$ and should “see” the rest of the circuit as $r=50\Omega$
- The output impedance of the attenuator should be 50Ω
- The load is $r=50\Omega$
- The desired attenuation is G

AC - circuits

- AC analysis of circuits containing capacitors and inductors

$$I = C \frac{dV}{dt}$$

$$U = L \frac{dI}{dt}$$

- Using complex numbers in electronics


- Impedance $Z_C = \frac{1}{j\omega C}$ $Z_L = j\omega L$

- Voltages and currents

$$U = U_0 e^{j(\omega t + \varphi)}, U_{MEASURED} = \text{Re}(U_0 e^{j(\omega t + \varphi)}) = U_0 \cos(\omega t + \varphi)$$

$$I = U/Z, \dots$$


Low pass filter

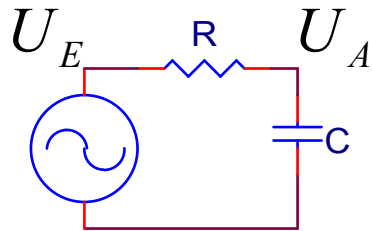


$$\frac{U_A}{U_E} = \frac{Z_C}{R + Z_C} = \frac{1/j\omega C}{R + 1/j\omega C} = \frac{1}{1 + j\omega RC} = \frac{1}{1 + j\omega\tau} \quad \text{pole}$$

$$\left| \frac{U_A}{U_E} \right| = \frac{1}{\sqrt{1 + \omega^2 \cdot \tau^2}} = \frac{1}{\sqrt{1 + (\omega/\omega_c)^2}} = \frac{1}{\sqrt{1 + (f/f_c)^2}}$$

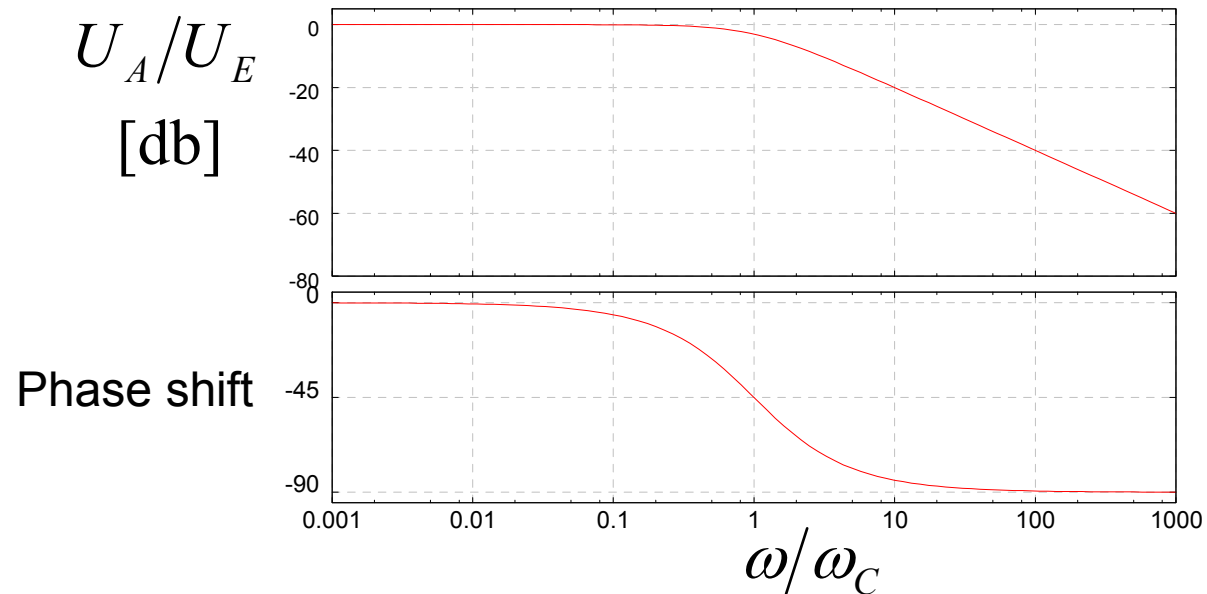where $\tau = R \cdot C$, $\omega_c = 1/\tau$, $f_c = \omega_c/2\pi = \frac{1}{2\pi RC}$




High pass filter

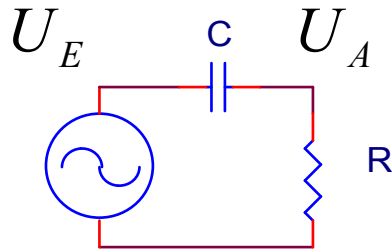


$$\frac{U_A}{U_E} = \frac{R}{R + Z_C} = \frac{R}{R + 1/j\omega C} = \frac{j\omega RC}{1 + j\omega RC} = \frac{j\omega\tau}{1 + j\omega\tau}$$

$$\left| \frac{U_A}{U_E} \right| = \frac{\omega\tau}{\sqrt{1 + \omega^2 \cdot \tau^2}} = \frac{\omega/\omega_C}{\sqrt{1 + (\omega/\omega_C)^2}} = \frac{f/f_C}{\sqrt{1 + (f/f_C)^2}}$$

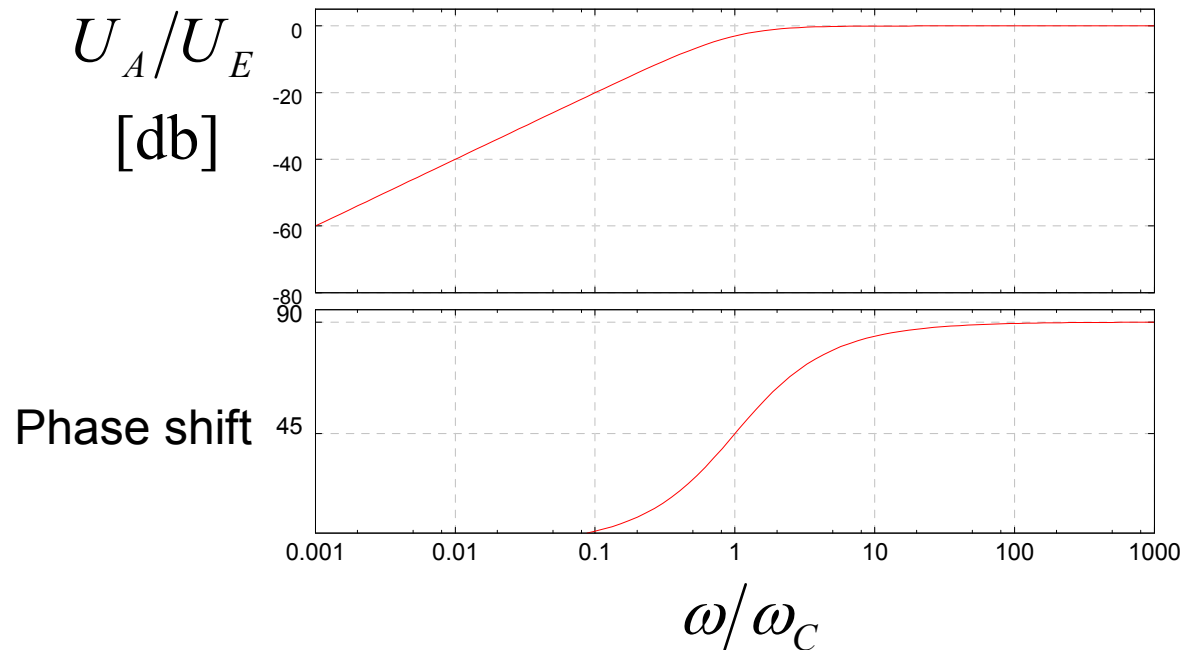where $\tau = R \cdot C$, $\omega_C = 1/\tau$, $f_C = \omega_C/2\pi = \frac{1}{2\pi RC}$



Pole/Zero correction

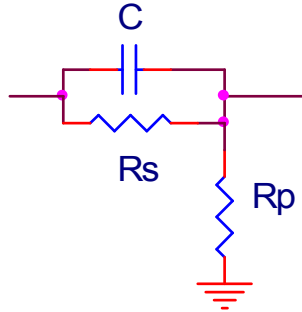

$$\tau_1 = R_S \cdot C, \quad \tau_2 = (R_S \parallel R_P) \cdot C$$


$$\frac{U_{OUT}}{U_{IN}} = K_0 \cdot \frac{1 + j\omega\tau_1}{1 + j\omega\tau_2}$$

← zero
← pole


$$K_0 = \frac{R_P}{R_S + R_P}$$

$$\tau_2 < \tau_1$$

!

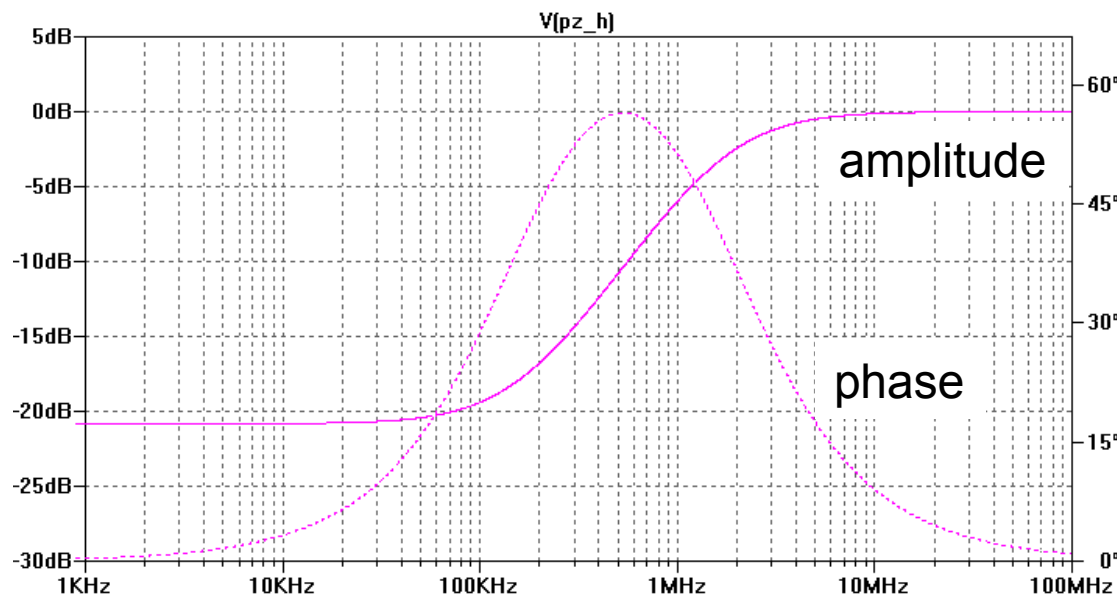

Practical realisation

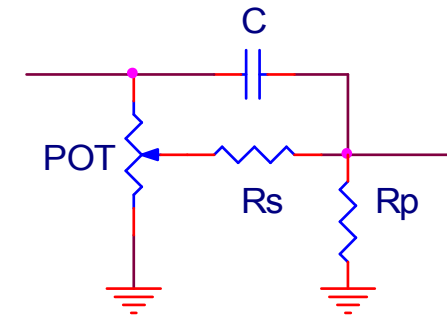


when $POT \ll R_S$

$$\tau_1 = R_S \cdot C \dots \infty$$

$$\tau_2 = (R_S \parallel R_P) \cdot C$$

Pole/Zero correction

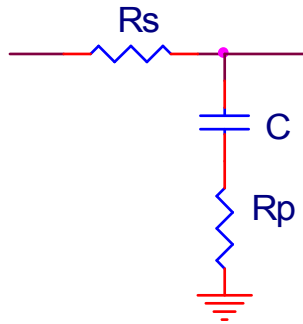

$$\tau_1 = R_P \cdot C, \quad \tau_2 = (R_S + R_P) \cdot C$$

$$\frac{U_{OUT}}{U_{IN}} = K_0 \cdot \frac{1 + j\omega\tau_1}{1 + j\omega\tau_2}, \quad K_0 = 1$$

$$\tau_2 > \tau_1$$

!

