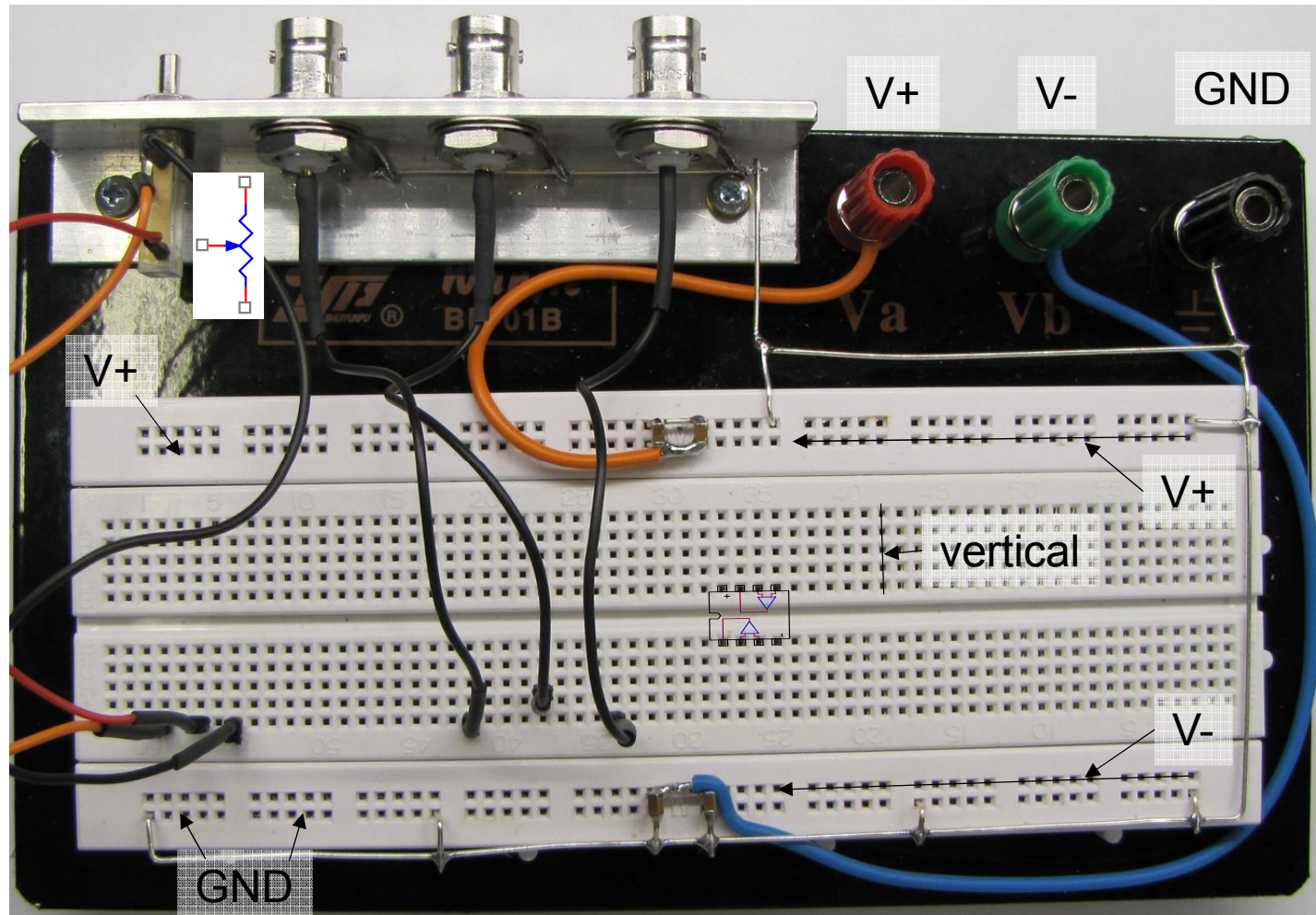


Common part

- Simple RC and CR networks
- Signal propagation
- Operational Amplifiers
 - Non-inverting
 - Inverting
- Triangle generator with Schmitt trigger and Integrator
- Discriminator with comparator



The breadboard




Simple RC and CR circuits

Investigate simple RC and CR networks
measure the

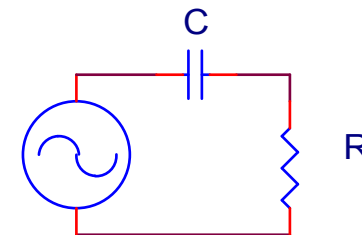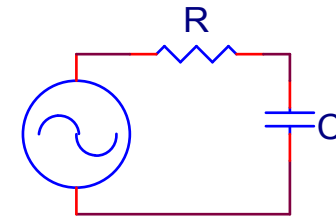- Attenuation and phase shift at 1Hz, 10Hz, ...100kHz, 1MHz with sinus input signal
- Rise/fall time using 1Hz rectangular input signal
- Identify low pass and high pass filter
- Construct a bandpass filter from both




Simple RC and CR circuits

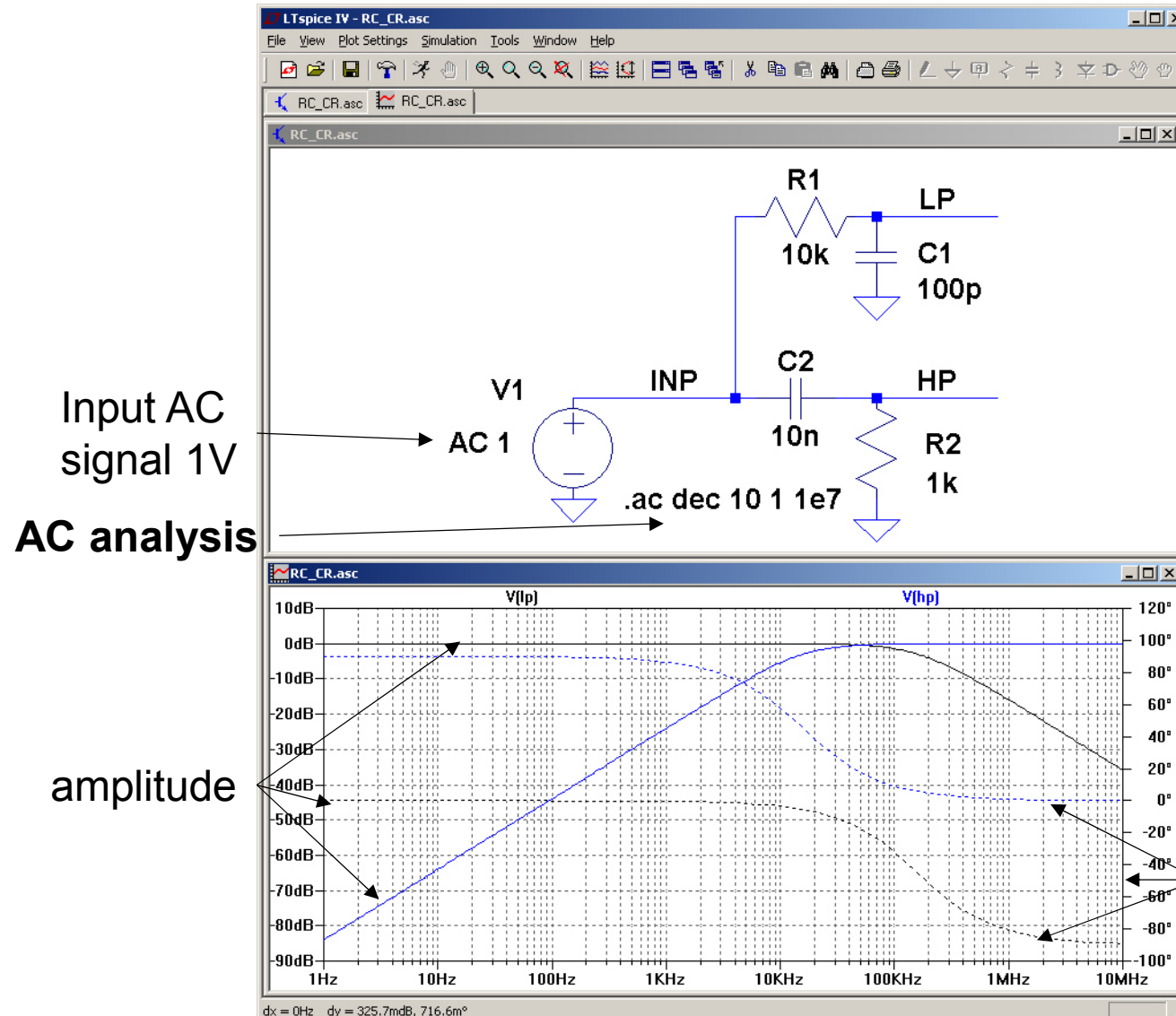


F3 – draw wire
 F6 – duplicate
 F7 – move
 F8 – drag
 F9 – undo
 Space – zoom fit
 Place:
 R – resistor
 C – capacitor
 L – inductor
 G – gnd
 F2 – component
 F4 – label net
 Ctrl-E – mirror
 Ctrl-R – rotate

Simple RC and CR circuits

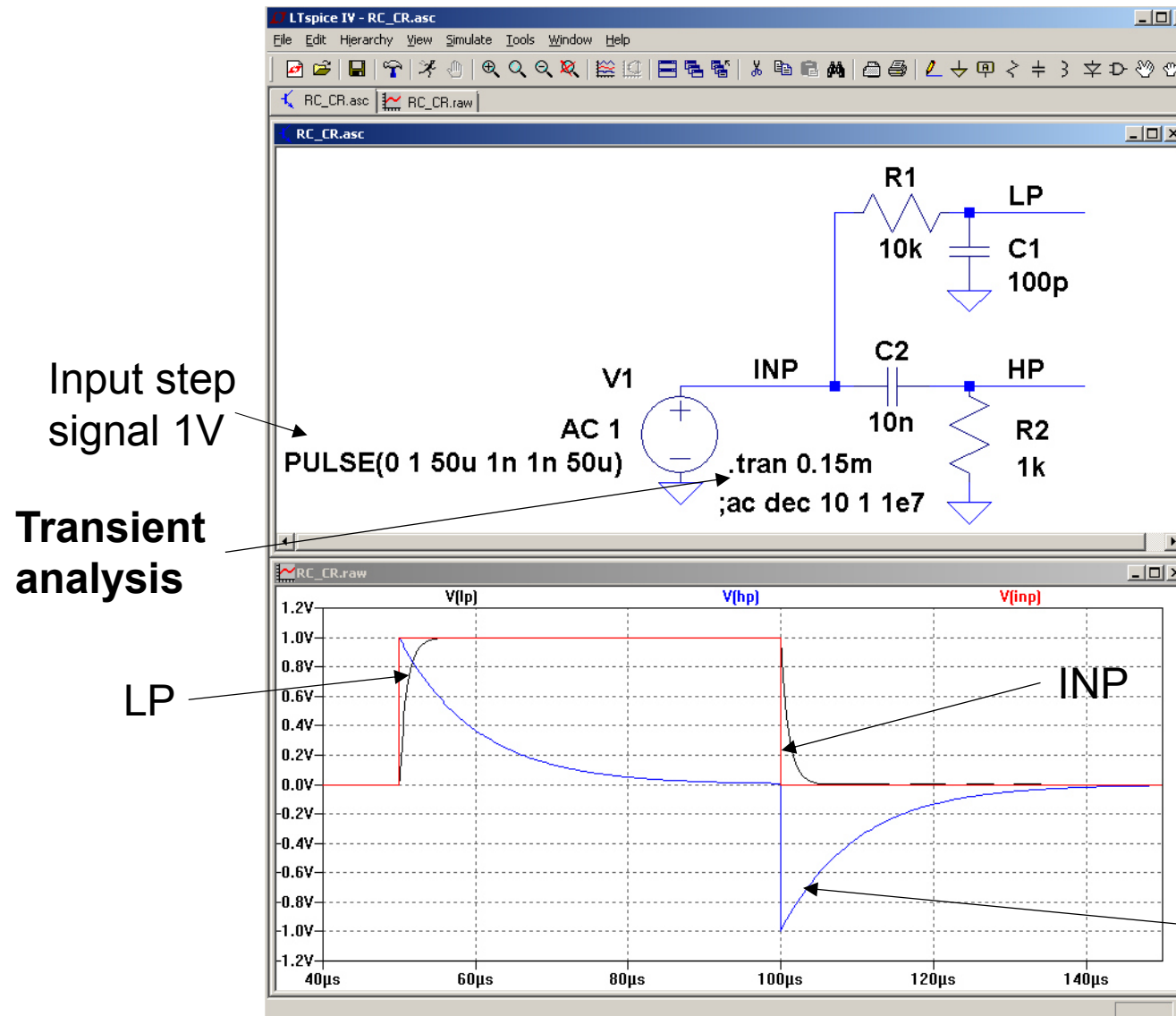

F3 – draw wire
 F6 – duplicate
 F7 – move
 F8 – drag
 F9 – undo
 Space – zoom fit
 Place:
 R – resistor
 C – capacitor
 L – inductor
 G – gnd
 F2 – component
 F4 – label net
 Ctrl-E – mirror
 Ctrl-R – rotate

Simple RC and CR circuits

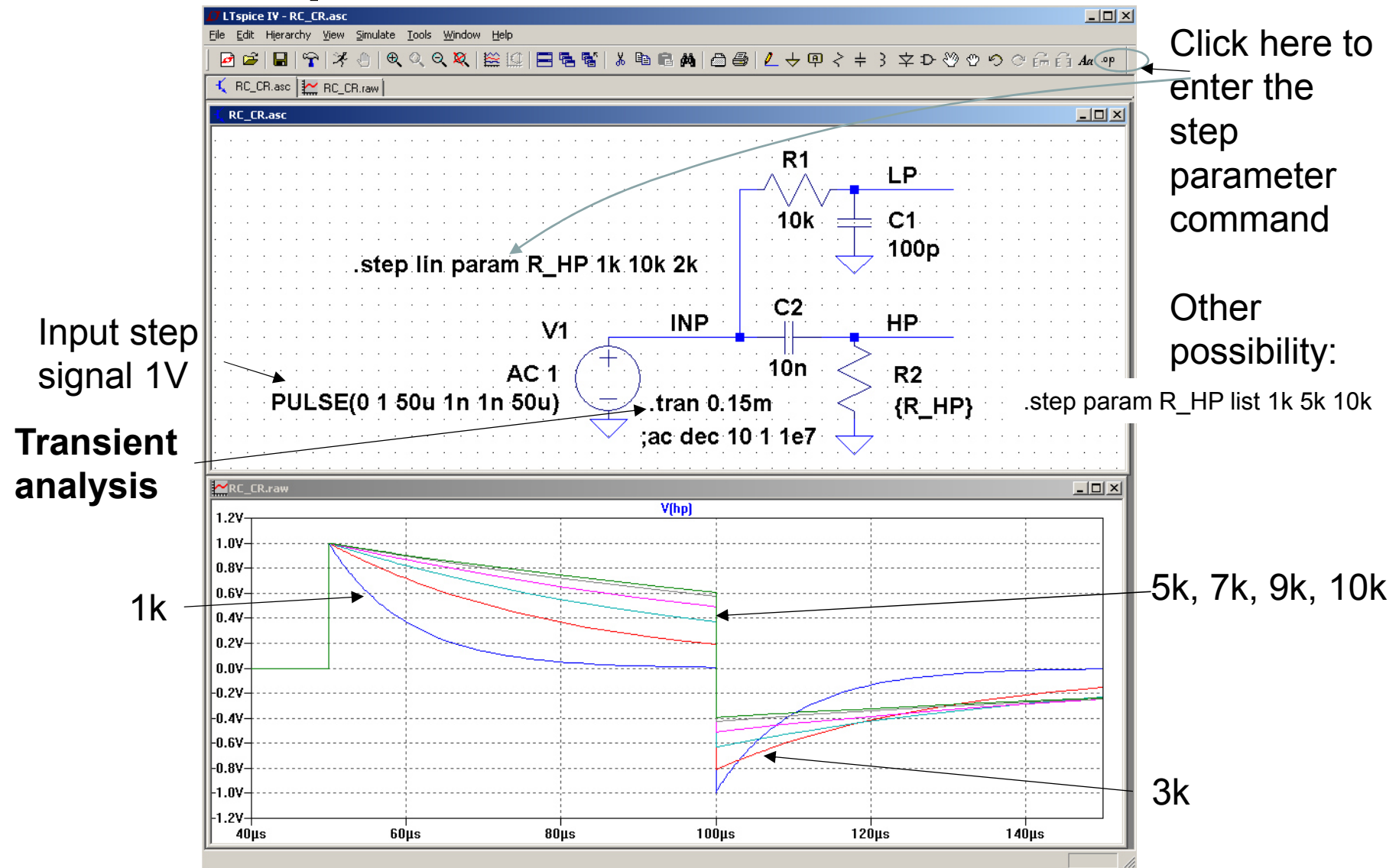

Signal propagation


Investigate a piece of coaxial cable (50Ω)

- With the cable from the generator to the oscilloscope and
 - with 50Ω termination
 - with other termination
 - without termination


measure the waveform

- with the shortest rise/fall time
- with longer rise/fall time


and try to explain the results

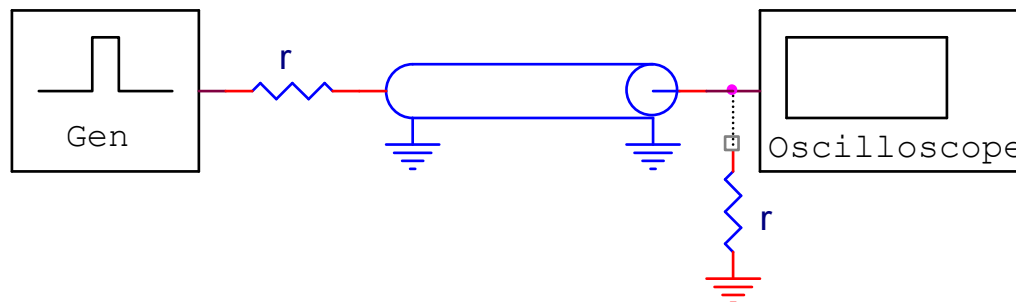


Signal propagation (2)

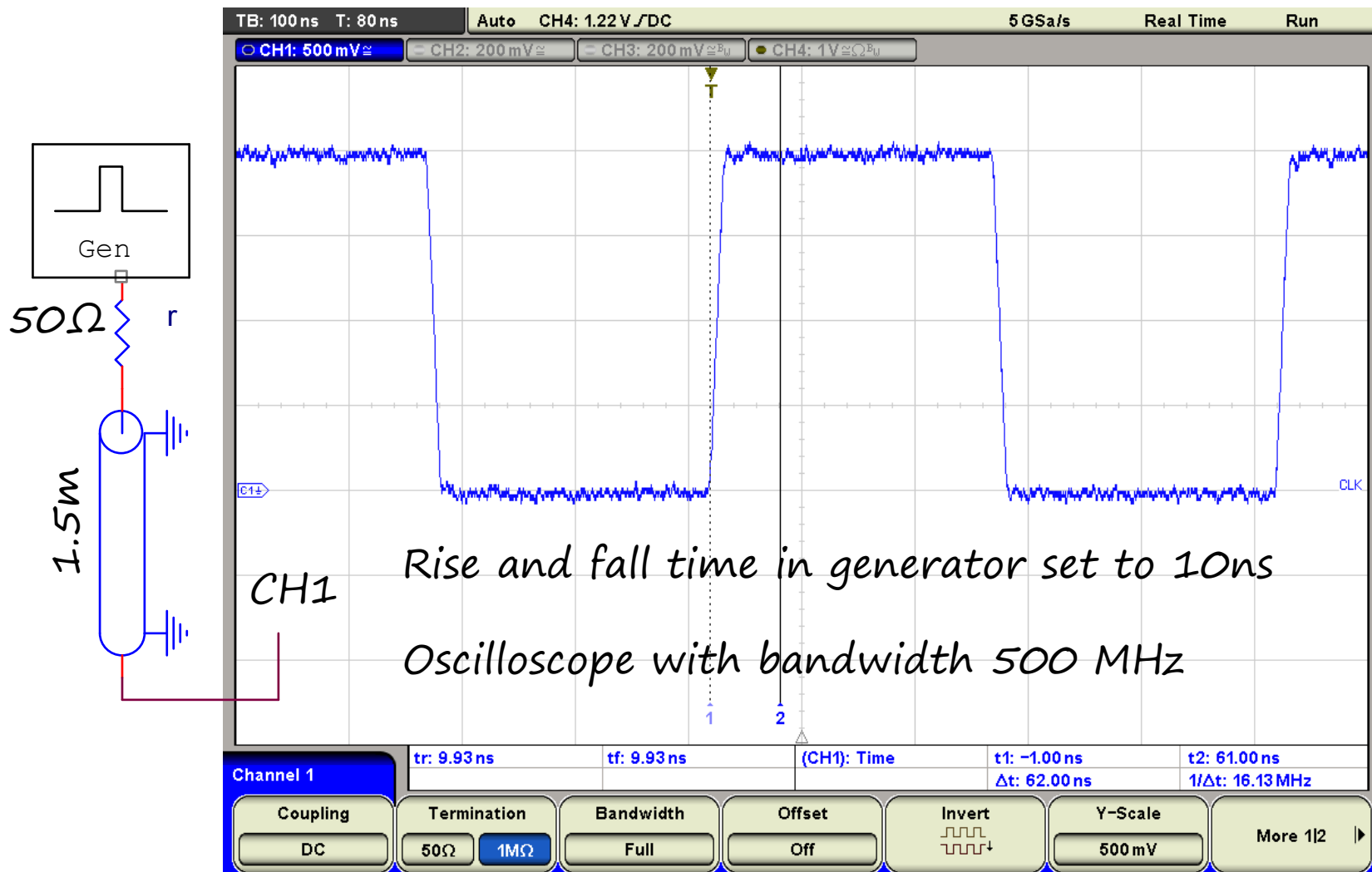

Signal propagation (3)

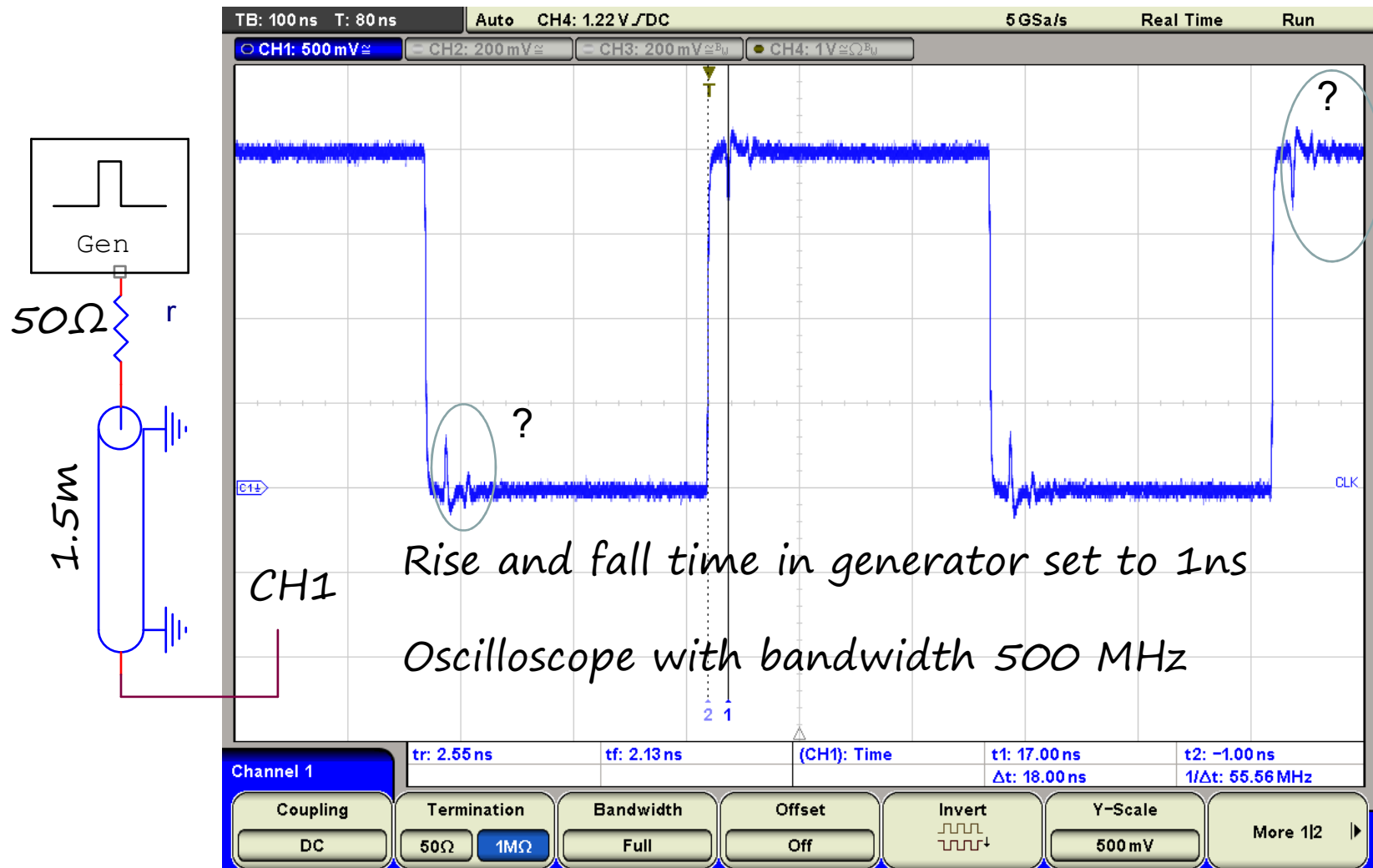

Signal propagation (4)

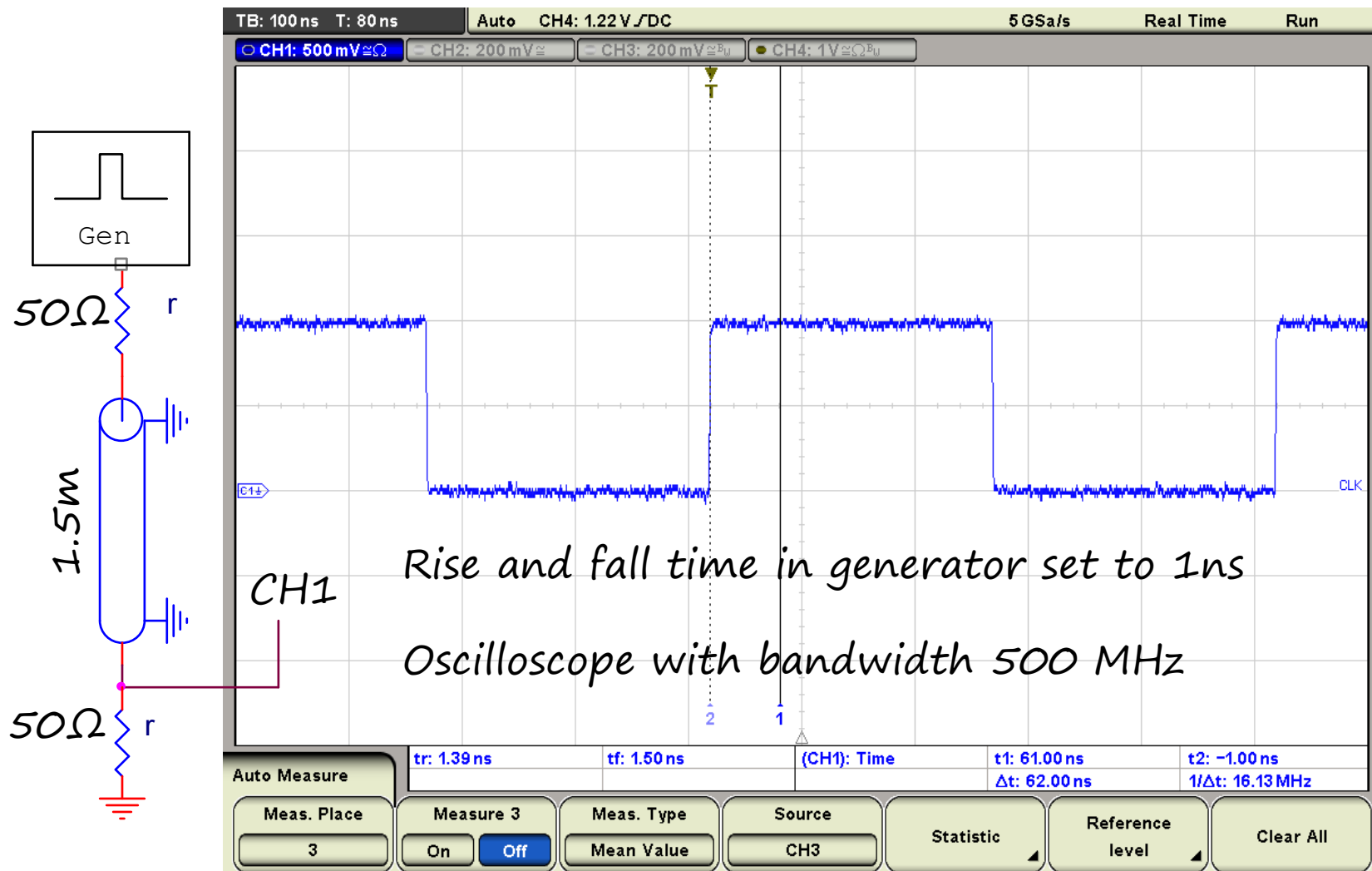


Signal propagation (5)


Investigate two pieces of coaxial cable (50Ω)

- With two cables as shown below and
 - with 50Ω termination
 - with other termination
 - without termination
 - with short

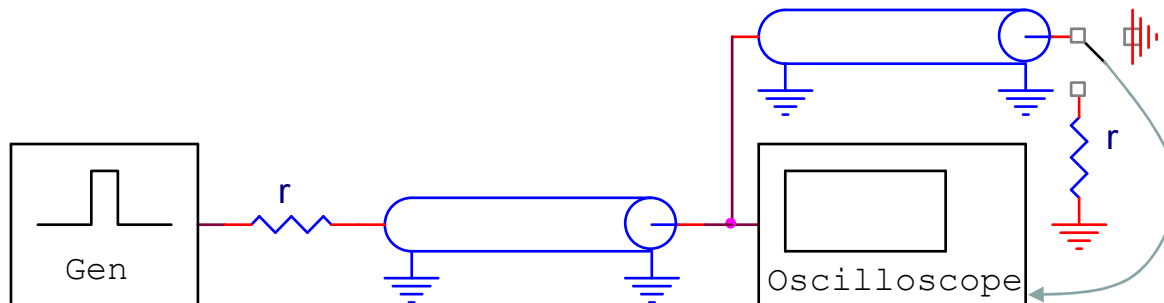
at the far end of the second cable measure the waveforms and try to explain the results





Signal propagation (6)

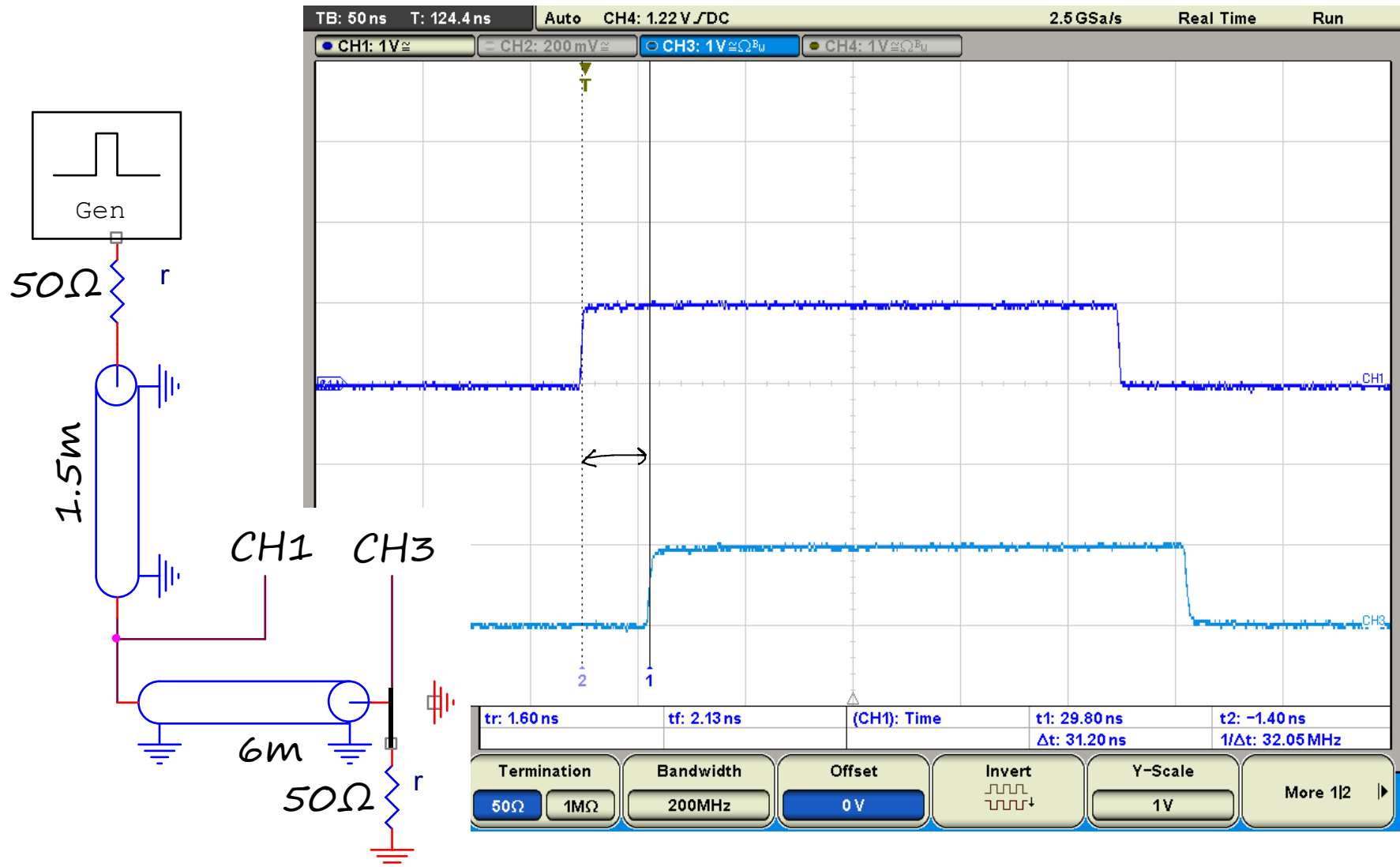

Signal propagation (7)

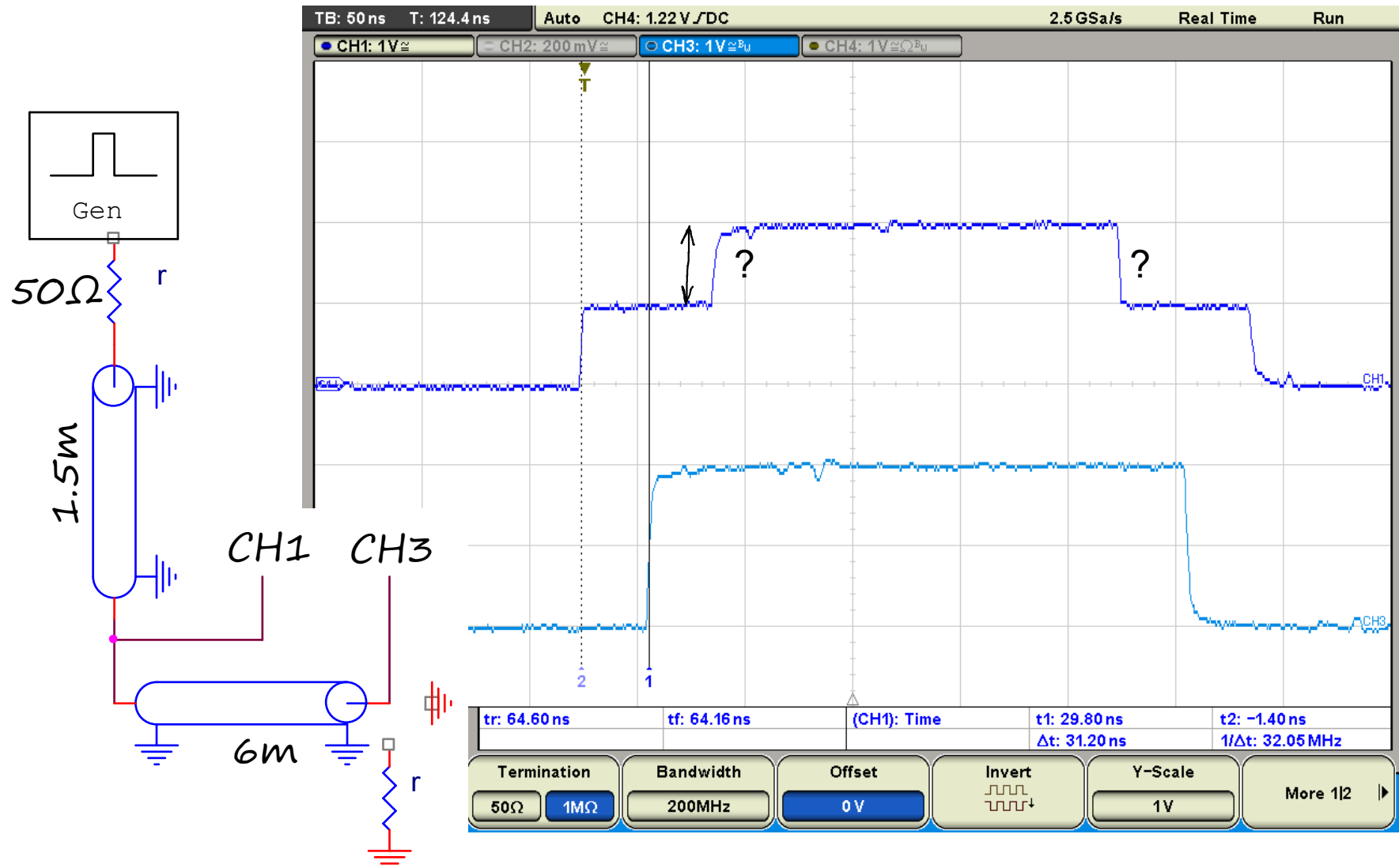


Signal propagation (8)

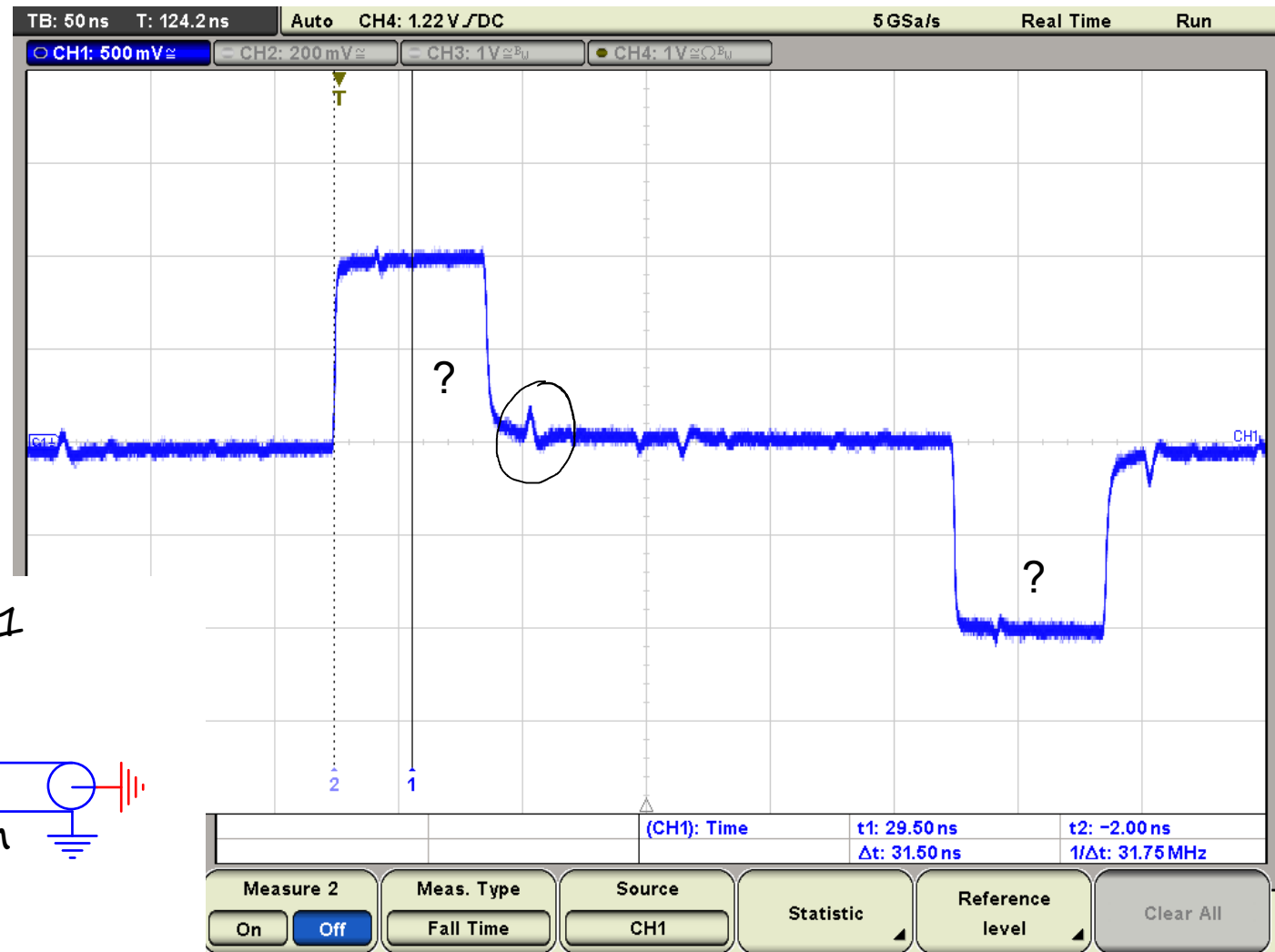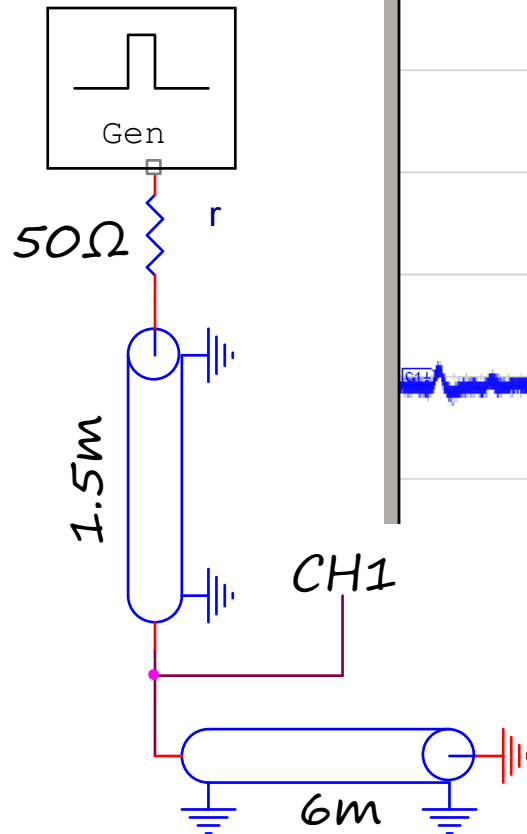


Signal propagation - conclusions

- The fastest component of a signal is its *rise/fall time* T_R
- The characteristic time of a piece of cable is the *transit time* T_T , for typical coaxial cable about 5 ns/m
- If $T_R \gg T_T$, the signal is slow and probably the only trouble could arise from the *cable capacitance* (typically around 100 pF/m)
- For fast signals a proper termination corresponding to its *characteristic impedance* is necessary, to avoid signal degradation

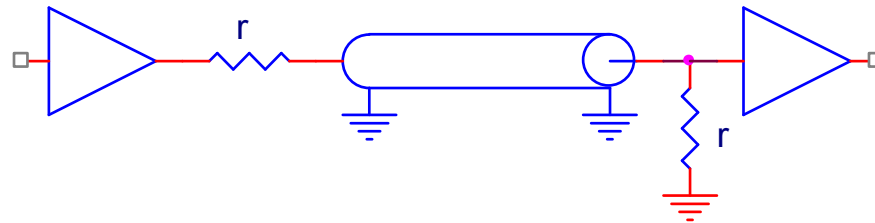

Operational Amplifiers

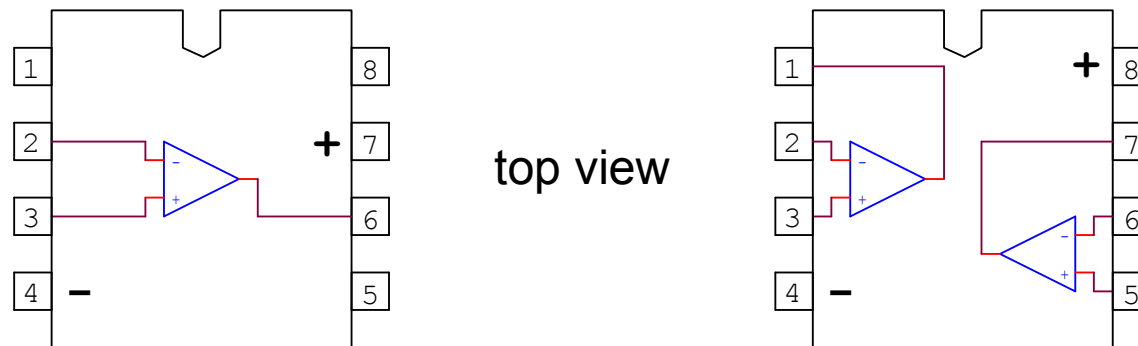- Ideal and real voltage feedback amplifier (VFA) - parameter
- Negative feedback with VFA
 - Non-inverting amplifier – offset, bandwidth, slew rate
- Positive feedback
 - Schmidt trigger, oscillator
 - Discriminator



Standard Pin-out of single and dual OA in a 8-pin package (DIL-8 or SOIC-8)

Operational Amplifiers in Simulator

LTspice comes with models from Linear Technology. In order to simulate an Op Amp from other manufacturer:

- Using google or a search on the manufacturer web page find a spice simulation model of the Op Amp – this must be a text file – check this with an text editor!
- Instantiate *opamp2* from the [Opamps] directory
- In symbol properties change the line with **value** containing *opamp2* with the name of the file containing the model, e.g. *TL071.lib*
- In the schematic sheet add a spice directive with `.op` like
`.inc TL071.lib` or `.lib TL071.lib`
- Copy the file with the simulation model in the project directory with the proper name (here TL071.lib)


Non-inverting amplifier

For gain=1, ≈ 10 , ≈ 100

- Calculate the resistors R1, R2
- Measure the offset voltage (only at Gain ≈ 100)
- Estimate the input bias current


measure the

- Gain at 1Hz, 1kHz, 100kHz, 1MHz with small signal sinus (output amplitude = 5% of the full range at 1 Hz) and if possible with large signal sinus (output amplitude = 90% of the full range at 1Hz)
- Output impedance – combine with the previous measurement + measure the output amplitude with proper load (e.g. 1k)
- Rise/Fall time, slew rate and settling time to 1% of the step using 1Hz rectangular input signal and output amplitude 5% and 90% of the full range; repeat the measurements with 100pF capacitive load at the output



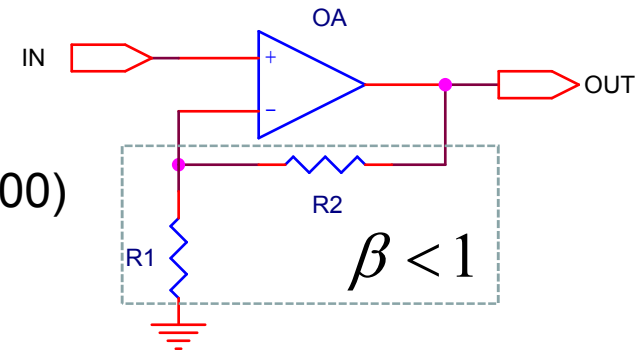


$$K_{\beta} = \frac{U_{OUT}}{U_{IN}} \approx 1 + \frac{R_2}{R_1} = \frac{1}{\beta} \geq 1$$

Definitions

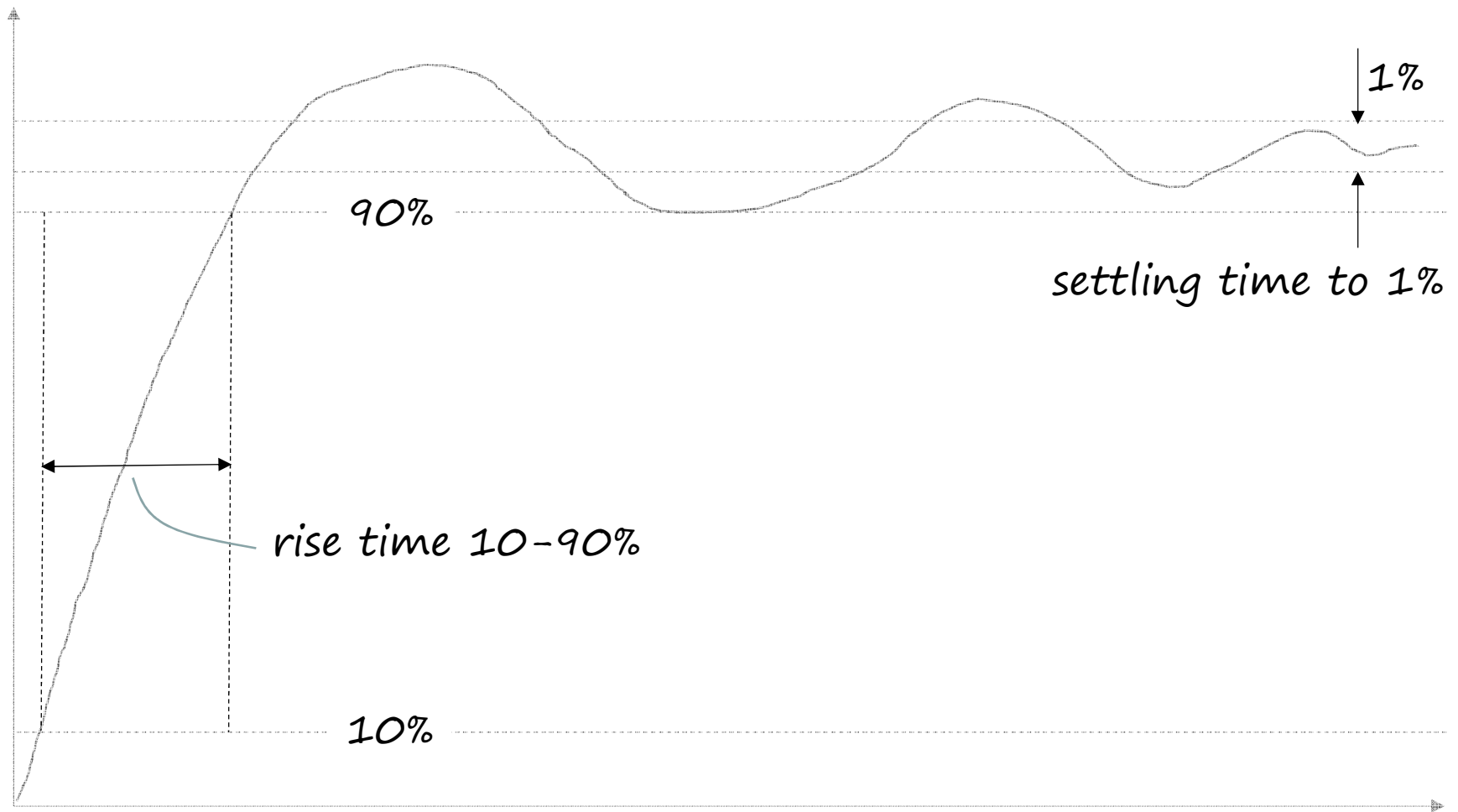


Non-inverting amplifier

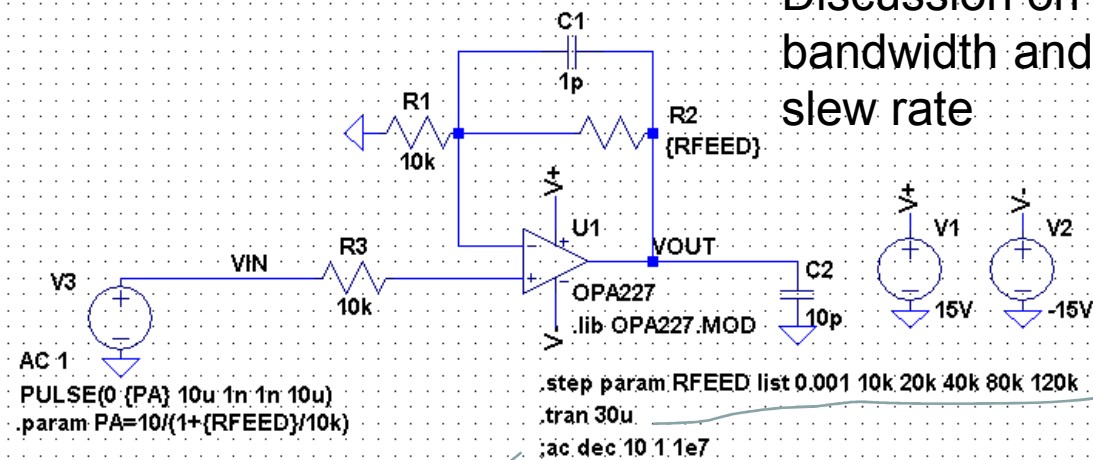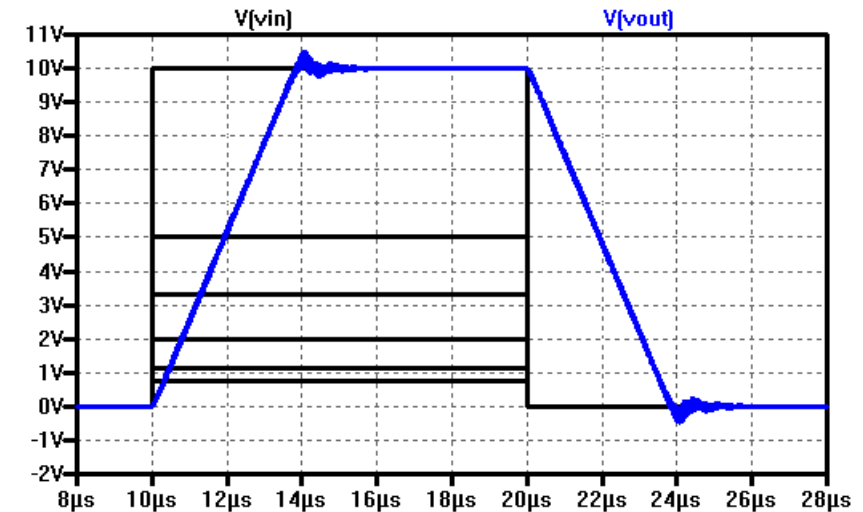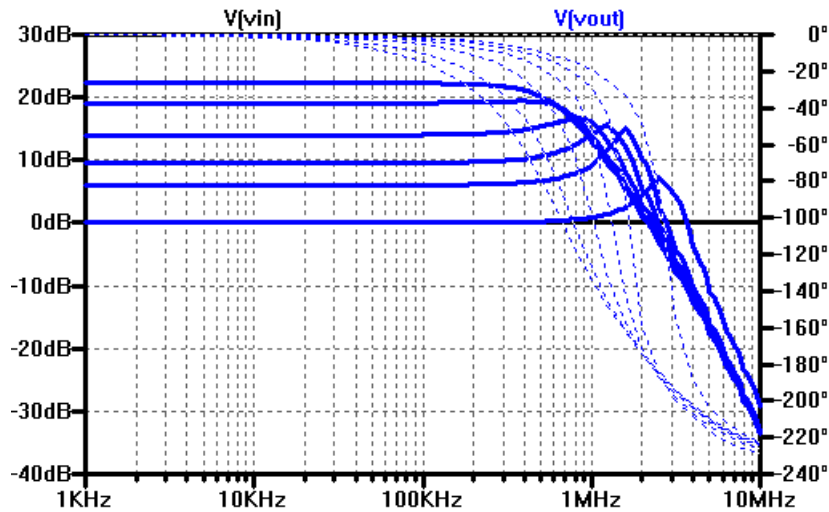

Inverting amplifier


For gain=-1, -10, -100

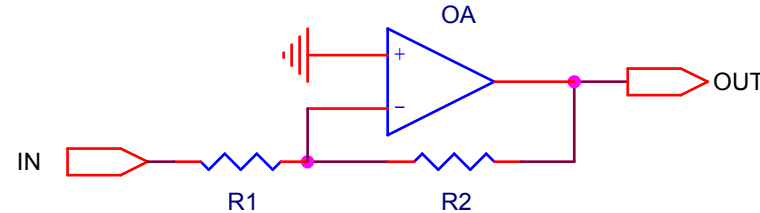- Calculate the resistors R1, R2
measure the




$$K = \frac{U_{OUT}}{U_{IN}} = -\frac{R_2}{R_1}$$

- Gain at 1Hz, 1kHz, 100kHz, 1MHz with small signal sinus (output amplitude = 5% of the full range at 1 Hz) and if possible with large signal sinus (output amplitude = 90% of the full range at 1Hz)
- The signal at the “virtual ground” – the negative input of the OA while measuring the Gain and again with rectangular input signal and output amplitude about 90% of the full range Influence of the osc-probe?
- For Gain=10 add a capacitor in the feedback so, that the bandwidth is limited to 10kHz; measure the Gain at 1Hz, 1kHz, 10kHz, 100kHz using sinus input signal; measure the rise/fall time using rectangular input signal

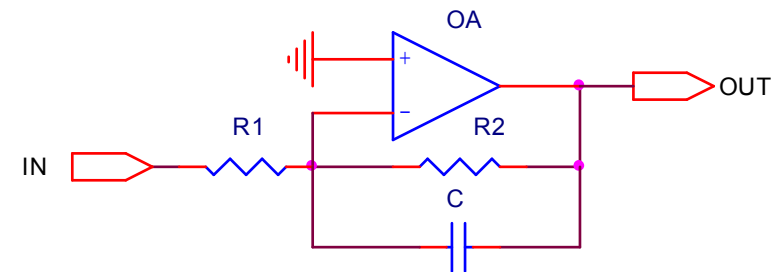

Triangle generator using comparator and integrator


OPTIONAL!

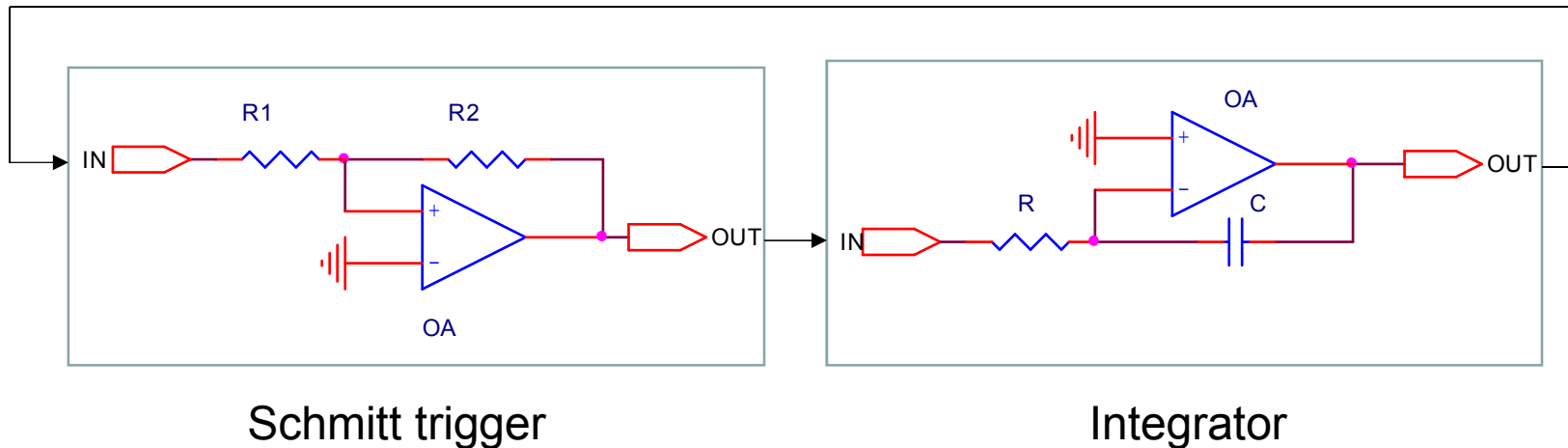

- Select the values of R1, R2, R and C in order to get frequency about 1 kHz and output range -10..+10V
- How can be varied only the frequency of the output signal?
- How can be varied only the amplitude of the output signal?

Use OPA2227 or OPA2277 or TL082

Comparator

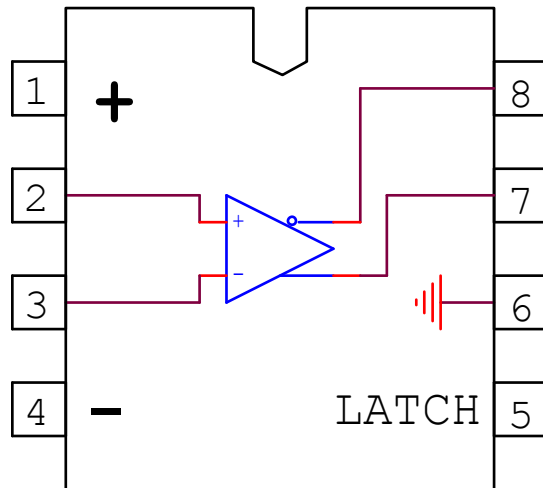


top view

AD8561, LT1016

Warning, the pin-out is NOT so standardized as for the operational amplifier!

In Simulator: if the model is missing, find it in internet (text file!), open the text file in LTspice, go to the line with `.SUBCKT`, then right-click and select **Create symbol**. It is recommended then to edit the symbol, at least to set the proper pin-names. The symbol contains as attribute the absolute location of the model in the file system => remove the absolute path prefix. The generated symbol is by default saved in [AutoGenerated] sub-directory of the lib\sym\ directory of LTspice: ver. XVII in ...\\MyDocs\\LTspiceXVII\\, ver. IV in C:\\Program Files (x86)\\LTC\\LTspiceIV\\

Discriminator – basic idea

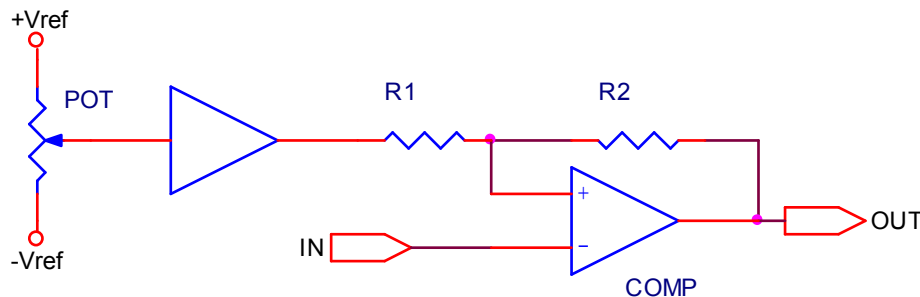

Preferably use a true comparator instead of Op Ampl in this experiment

Investigate the discriminator

- Vary the amplitude and the rise/fall times of the input signal
- Add some high frequency noise to the input signal using a second generator and capacitive coupling
- Adjust the hysteresis according to the noise level
- Measure the input to output delay at different input amplitudes

Applications:

- Single Channel Analyser (SCA)
- Time Over Threshold Analyzer
- Timing





Specific part

- Particle physics experiments
 - Shaping Amplifier and Pole/Zero correction
 - Single channel analyser (SCA)
 - Time over Threshold (ToT)
 - Timing with Leading Edge (LE) and Constant Fraction Discriminators (CFD)
- Optical experiments
 - Constant current sources
 - Temperature measurements
 - Photodiode amplifier
 - PID

Shaping Amplifier

- The preamplifier delivers normally long exponential pulses, which may overlap
- The later amplifier stages have several functions:
 - Invert the polarity if necessary
 - Shorten the pulses with fast return to zero
 - Amplify to a level proper for further processing
 - Shape optimal for the signal to noise ratio and for the further processing (digitization)
- Simulate and build a shaping amplifier, play with the P/Z correction and the shaping parameters (shaping time, gain), vary the delay between the two pulses to see the effect of overlapping


Shaping Amplifier

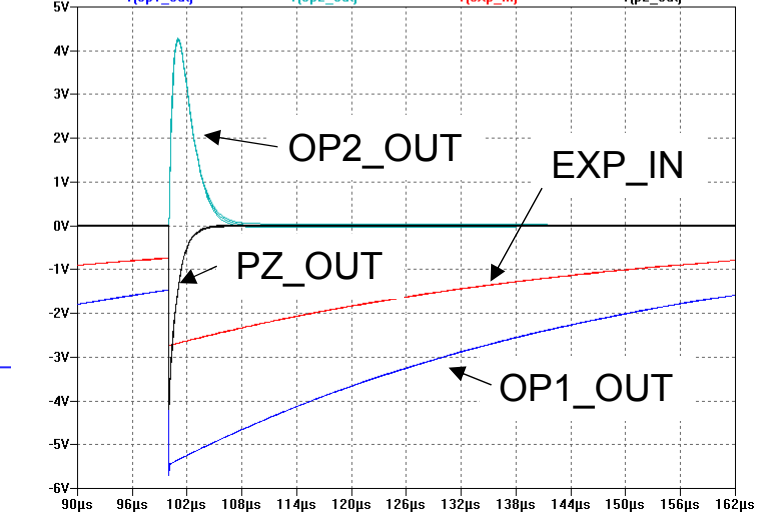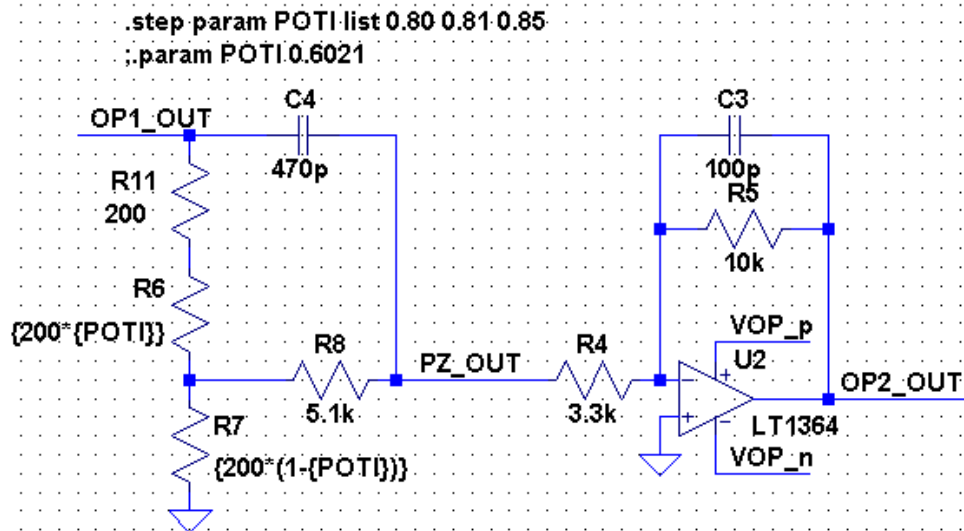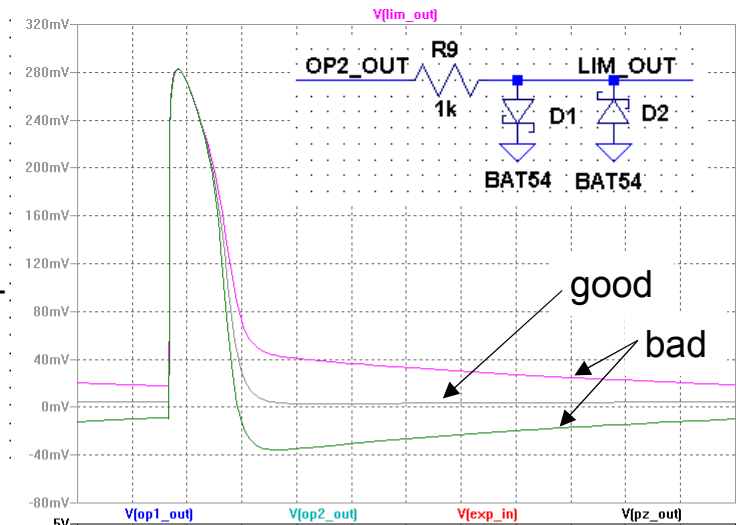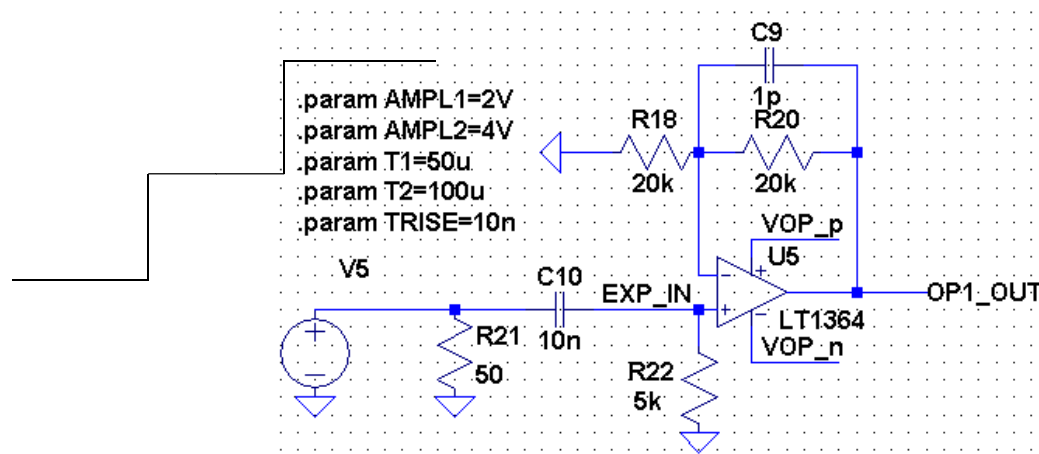

Possible OpAmp: LT1361 (slowest), LT1364, LM6172 (fastest)

Single Channel Analyzer

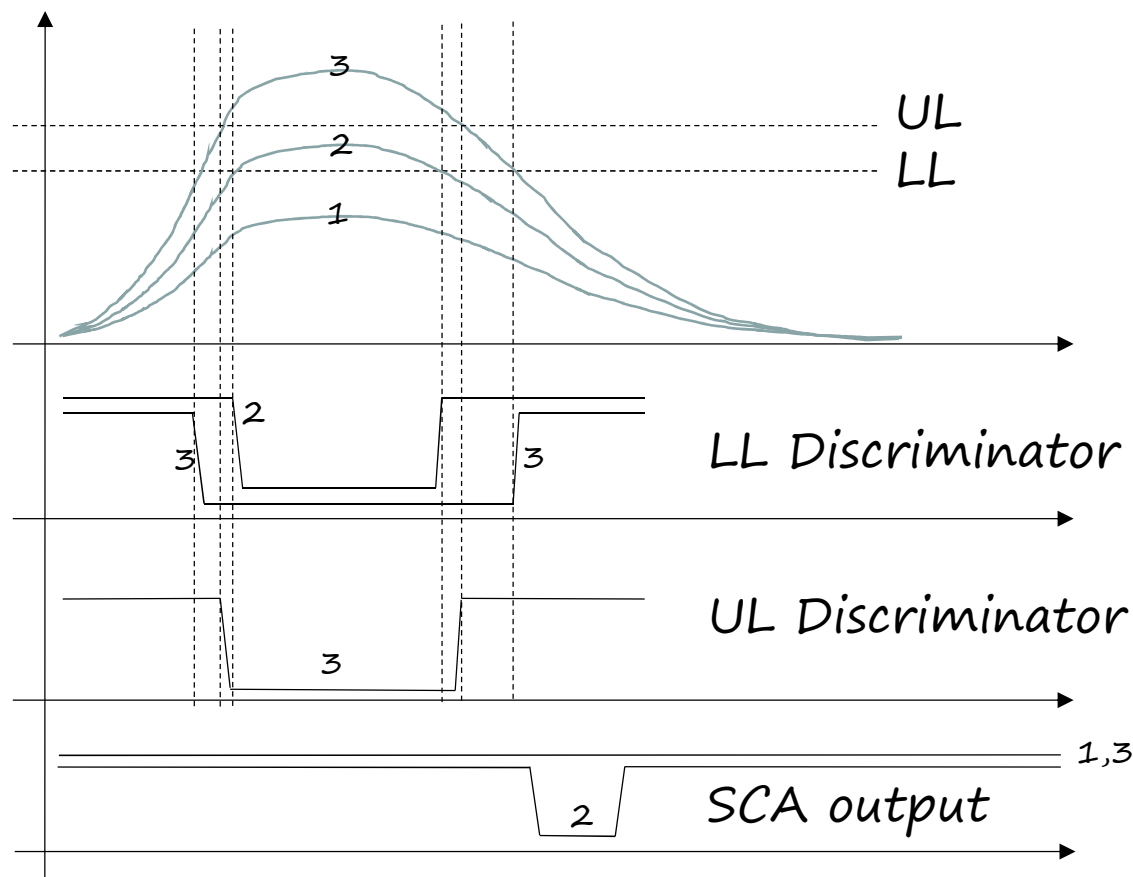Select pulses with amplitude in some programmable window




- Use two discriminators for the upper level (UL) and lower level (LL)
- Some logic takes the decision after both discriminators are inactive


Single Channel Analyzer

- Programmable lower level and window so that
 - the window can be moved through the whole range preserving the window size
- Build the upper level as lower level + window
- This is a primitive way to measure the amplitude spectrum of the pulses, but is simple! Normally the window position & width is optimized once and then the pulses are counted for long time

SCA – building blocks

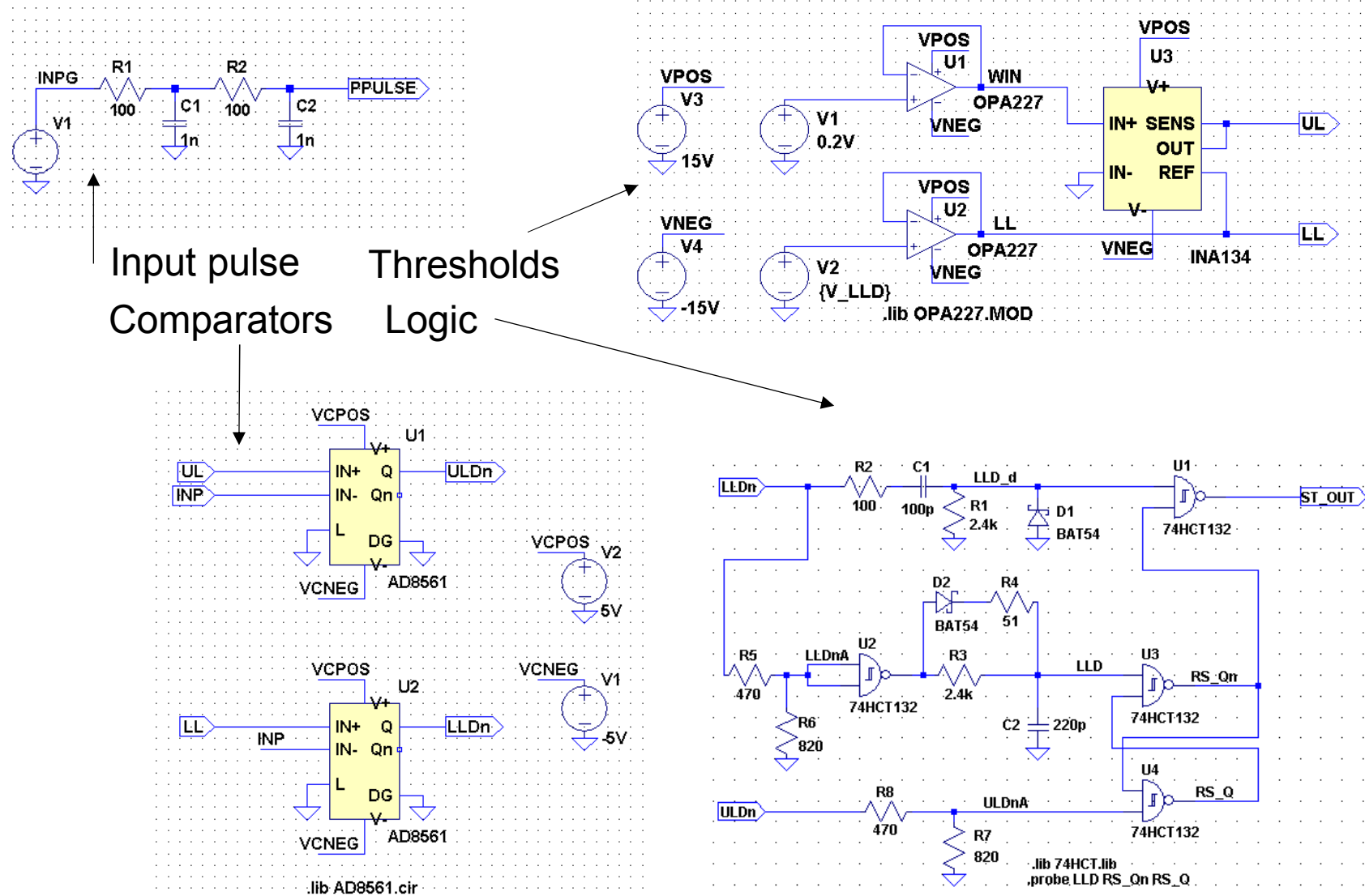


SCA – put all together

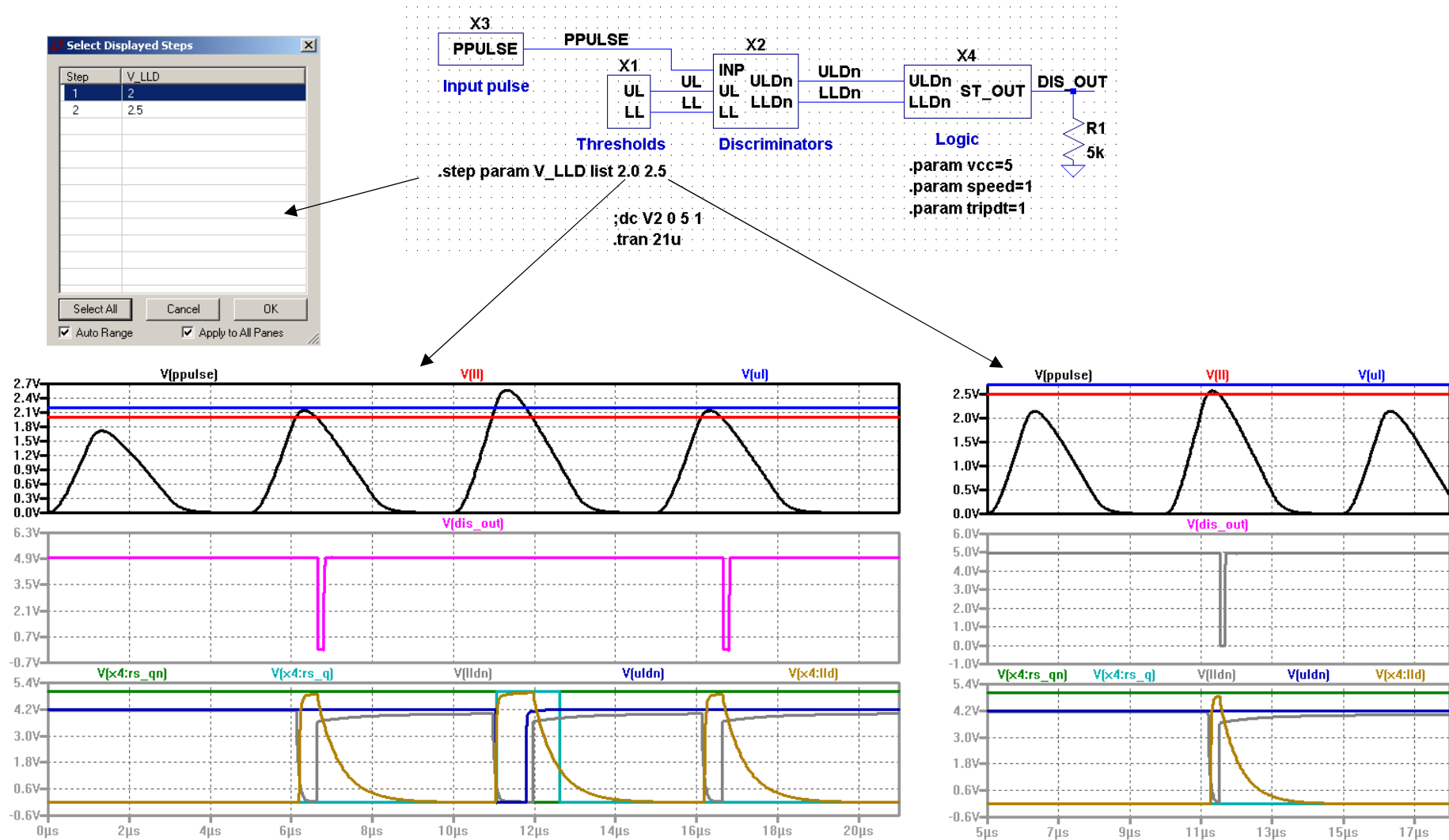

Discriminator – time over threshold (ToT)

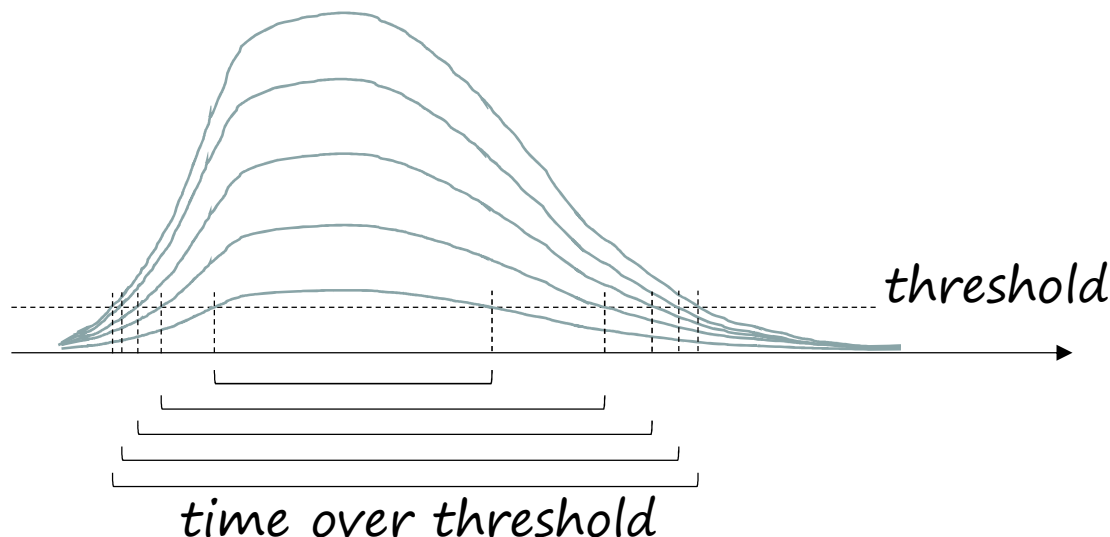- The idea is to measure roughly the amplitude of the pulses
- With a constant threshold, the time over the threshold is a function of the amplitude
- Provided the shape remains stable, the correlation ToT – Amplitude is non-linear but known




Discriminator – time over threshold

```

;step param VPULSE list 0.5 1.0 1.5 2.0 2.5
.step lin param VPULSE 0.4 3.0 0.2
.param V_LLD 0.3


```

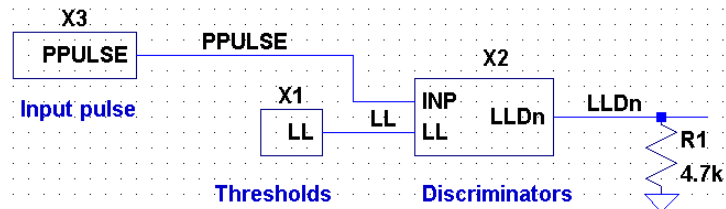

```


.meas tran pwidth trig V(lldn) val=2.0 fall=1 targ V(lldn) val=2.1 rise=1
.meas tran vp_max max V(ppulse)
;dc V2 0 5 1
.tran 6u

```

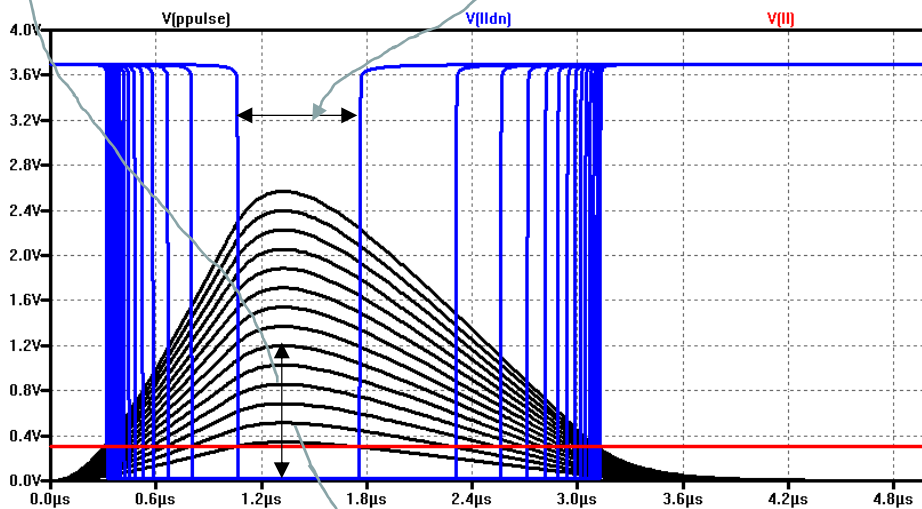

X3 – PPULSE is the same as in SCA
X1 and X2 – half-version of the SCA discriminator

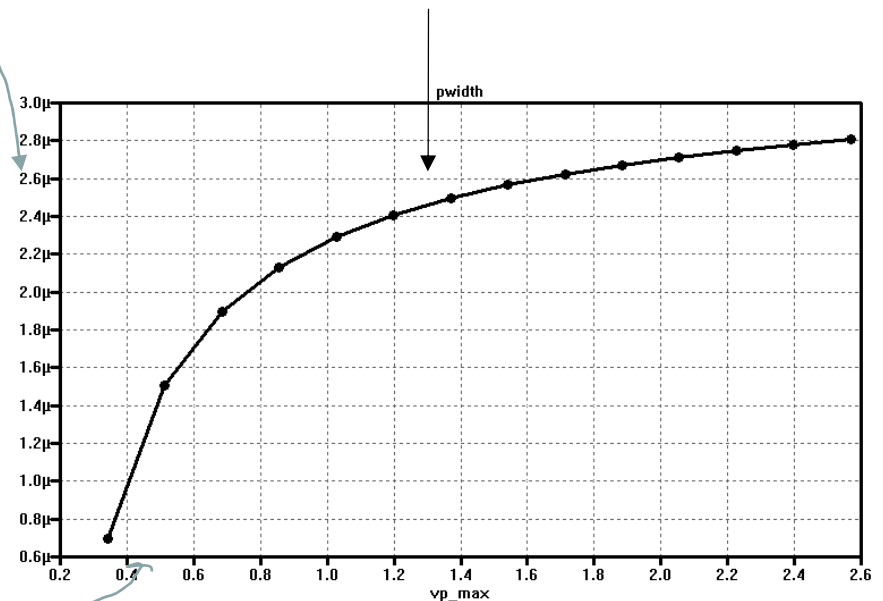
The dependence of the pulse width (the time over threshold) is non-linear and a function of the pulse shape!







Discriminator – leading edge timing

- The same circuit can demonstrate another typical task in detector experiments – timing
- When measuring the time distance between two detector pulses, the simplest way to get a digital start and stop signals is to use a discriminator with constant threshold
- What is the problem of this solution?


Improving the leading edge timing

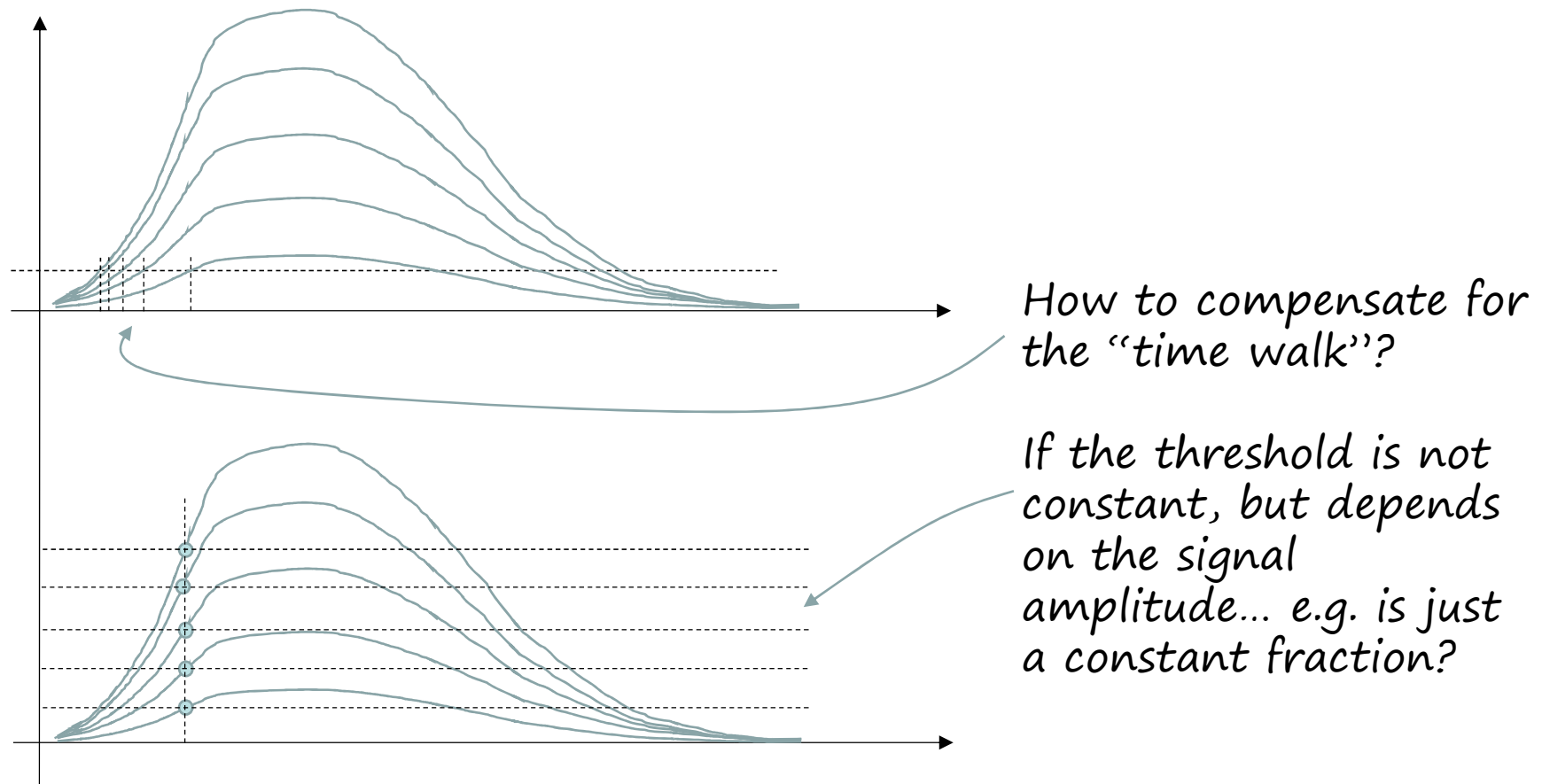

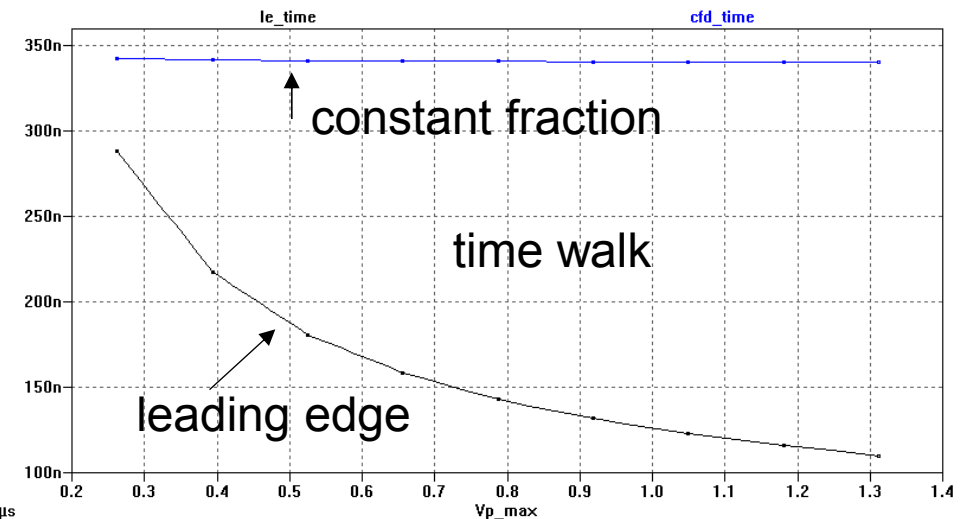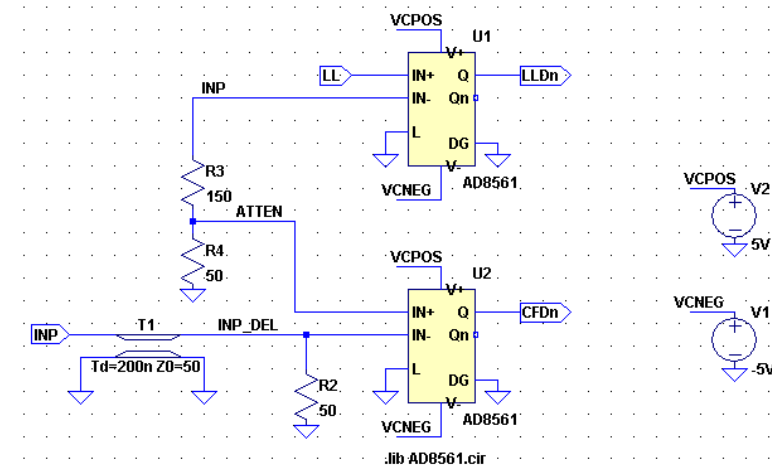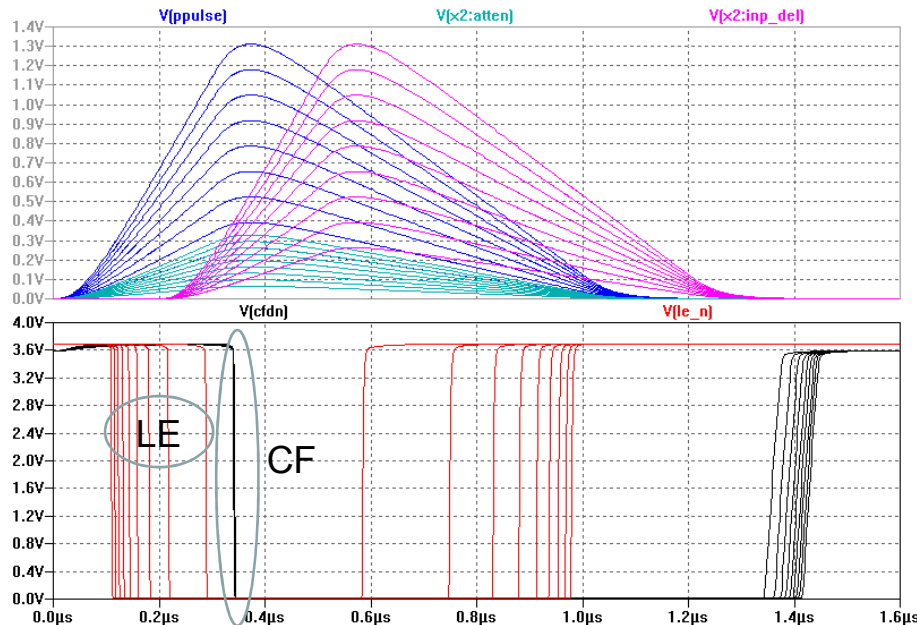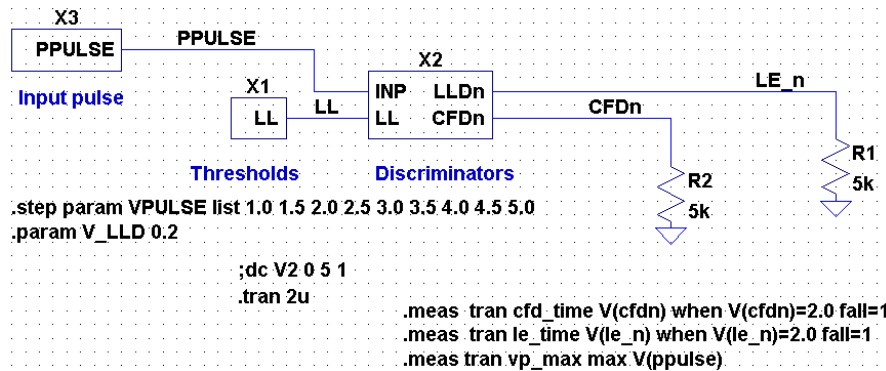Timing – leading edge vs. constant fraction



Solder your first board

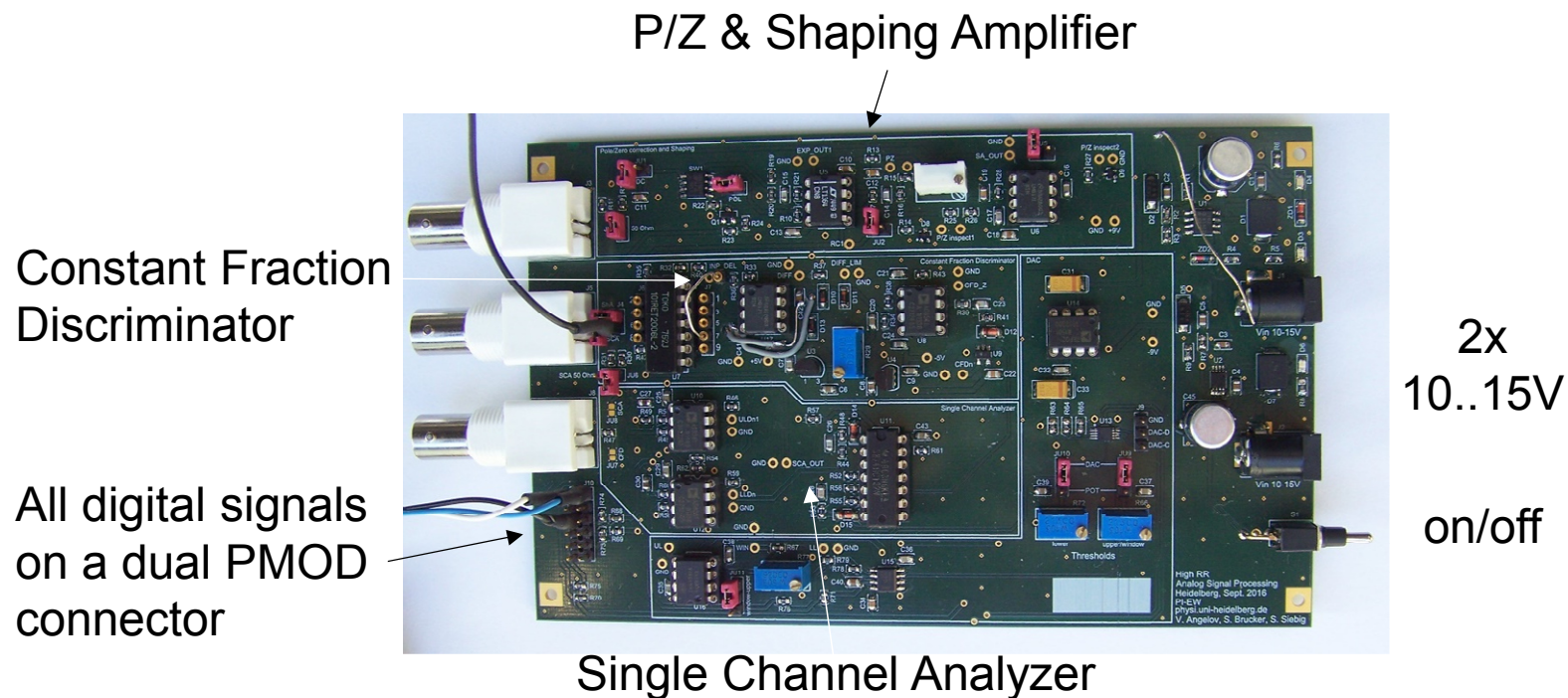

Thank you for your attention and patience!